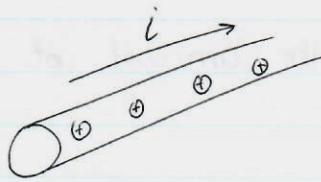


CURRENT

\Rightarrow Current direction is based on
④ charge movement

Mathematically:

$$\text{current } \vec{i} = \frac{dq}{dt} \leftarrow \begin{matrix} \text{charge (C)} \\ \times \text{time (s)} \end{matrix}$$

• To get q : integration


$$dq = i dt$$

$$\therefore q = q(t_0) + \int_{t_0}^{t_1} i(\tau) d\tau$$

To get all-time current, assume $t_0 = -\infty$ and $q(t_0) = 0$

$$\therefore q = \int_{-\infty}^{t_1} i(\tau) d\tau$$


Reference direction:

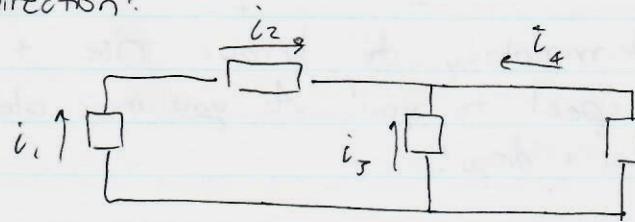


1. Choose current direction arbitrarily
2. If current val. is negative, reverse direction

Types:


DC

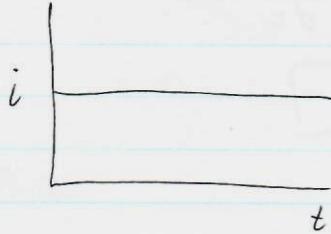

AC

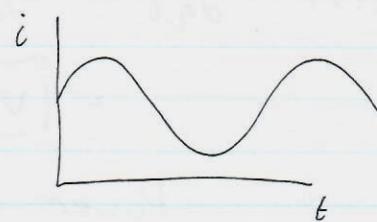

Time-varying

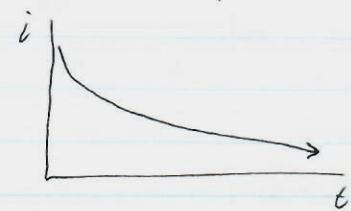

VOLTAGE

Think of voltage as the amount of work a single charge can do.


Mathematically:

$$V = \frac{dw(t)}{dq} \leftarrow \begin{array}{l} \text{work (J)} \\ \text{charge (C)} \end{array}$$

Voltage ($V_C = V$)


Much like current, find work via integration.

Preference polarities:

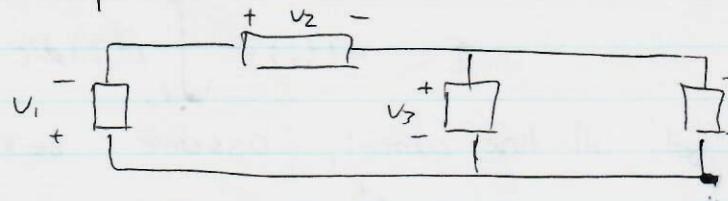

1. Put +, - to indicate high + to volt respect.
2. Arbitrary (negation rule like current)

- Can also use an arrow (- to +)

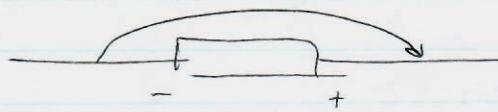


Quick terminology to know: rise + drop

↳ Respect to you! As you move along circuit, you have rises + drops!


POWER

$$P(t) = \frac{dw}{dq} \cdot \frac{dq}{dt} = \frac{dw}{dt} = \boxed{[V \cdot i]}$$

Power

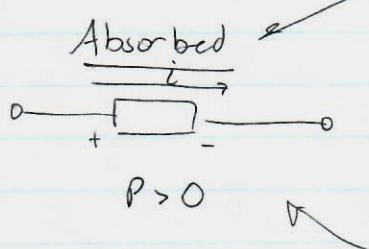

\Rightarrow Passive sign

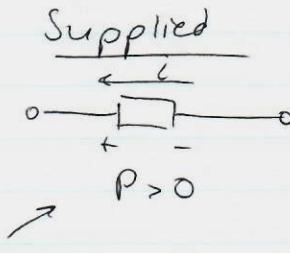


\nearrow Negative sign!

Energy conservation:

$$\sum \text{supplied pow} = \sum \text{absorbed pow}$$

To find energy from power: simple integration.

CIRCUIT BASICS

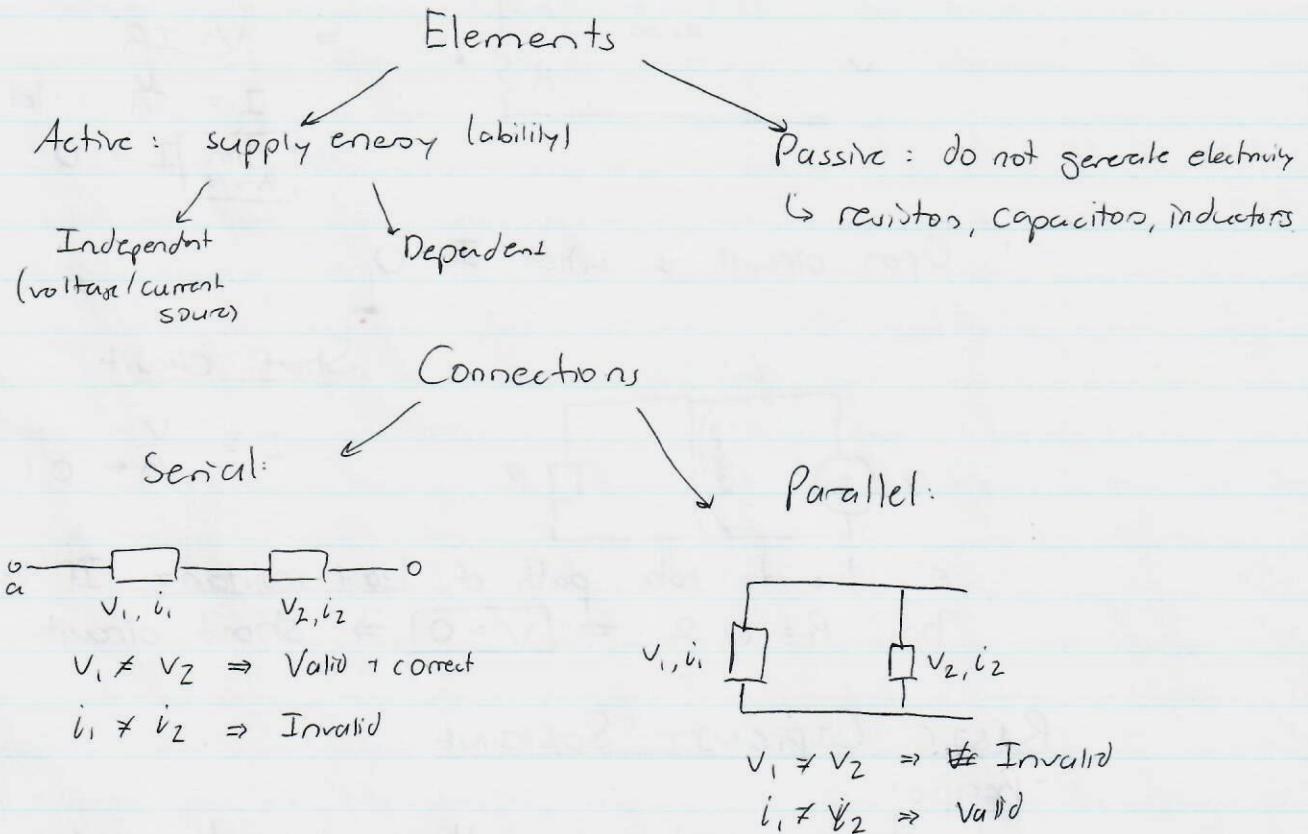

DEPENDENT SOURCES

$$\begin{cases} V = \alpha V_x \\ V = \alpha i_x \end{cases}$$

$$\begin{cases} i = \alpha V_x \\ i = \alpha i_x \end{cases}$$

RESISTORS



↳ Resistance: $R \geq 0, \Omega$


Ohm's Law = $V = I \cdot R$ (change into dif. forms: $\frac{V^2}{R}$ using power rule)

Conductance:

$$G = \frac{1}{R} \quad (\Omega^{-1} = \text{Siemens (S)})$$

Know how to express V, I, R, P in terms of G .

OPEN + SHORT CIRCUITS

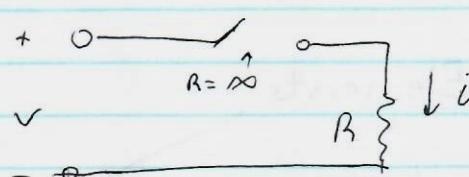


Open circuit

$$V = IR$$

$$I = \frac{V}{R} + \text{let } R \rightarrow \infty$$

$$\therefore \lim_{R \rightarrow \infty} I = 0$$

Open circuit is when $I = 0$.

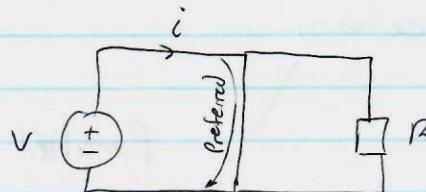

Short circuit

$$I = \frac{V}{R} \leftarrow 0!$$

e^- like to take path of least resistance. If the path has $R = 0 \Omega \Rightarrow V = 0$ \Rightarrow short circuit.

BASIC CIRCUIT SOLVING

- Recipe:



1. Assign unknown voltages, current, resistance.

↳ Use serial + parallel laws to simplify problem.

2. Resistor: use Ohm's Law.

3. Solve the system. w/ polarities in mind.

↳ Es: // Passive vs not passive current

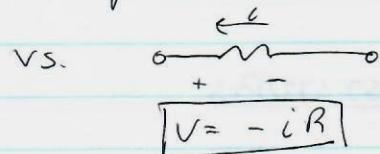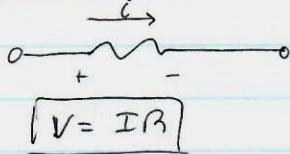

* Passive sign convention + Ohm's Law are extremely important. Follow this as dogma

KIRCHHOFF LAWS


1. Kirchoff's Current Law (KCL):

The sum of current at a node is 0.


$$\sum i_{in} = \sum i_{out} \quad (\text{assign polarity to currents})$$

ONLY @ node

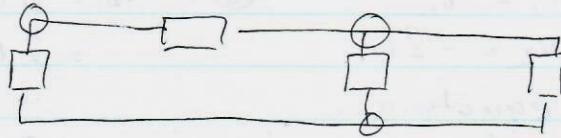Node: 2/more element connected at 1 point



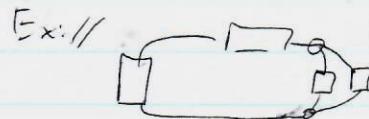Trick to finding nodes: take empty wires + try to remove as much as poss.



Ex: //

$$\Rightarrow \text{KCL: } i_1 = i_2 + i_3 + i_4$$

To solve circuit using only KCL:


$$\# \text{ of eq.} = \# \text{ of nodes} - 1$$

2. Kirchoff's Voltage Law (KVL):

The algebraic sum of voltages along a loop is 0

$$\sum V_{\text{loops}} = \sum V_{\text{nodes}}$$

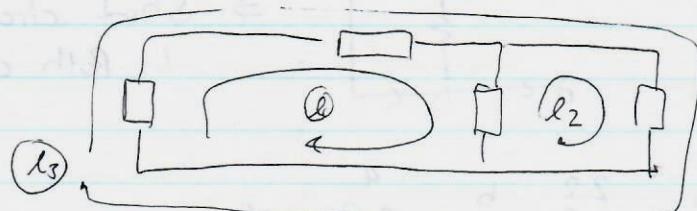
Loop: path where no element encountered more than once.




Loop \rightarrow mesh: loop w/ no inner loop (l_1, l_2 are meshes)

Solving circuit w/ KVL: $\# \text{ of eq.} = \# \text{ of meshes.}$

Note*:

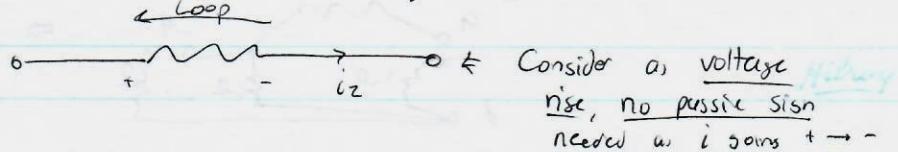

- Ex: //

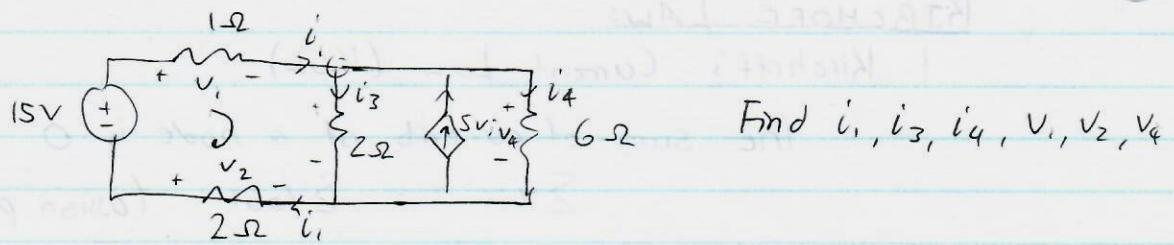

Find $i_1, i_3, i_4, v_1, v_2, v_4$

1. Ohm's law equations.

$$\textcircled{1}: v_1 = i_1$$

$$\textcircled{3}: v_4 = 6i_4$$

$$\textcircled{2}: v_2 = -2i_1$$

$$= 2i_3 \leftarrow 2\Omega \text{ resistor.}$$

2. Kirchhoff equations:


$$\text{KCL: } 5i_1 + i_1 = i_3 + i_4 \quad - \textcircled{4}$$

$$\text{KVL: } 15 + v_2 = v_1 + v_4 \quad - \textcircled{5}$$

Solve.


RESISTOR EQUIVALENCE

Series:

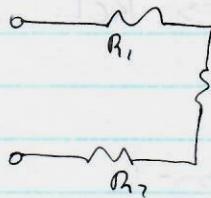

$$R_{eq} = R_1 + R_2 + R_3$$

Parallel:

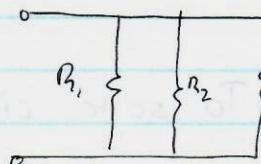


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\Rightarrow G_{eq} = G_1 + G_2 + G_3$$

- Common formula for 2 resistor parallel circuit:

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$


- Resistor short circuit:

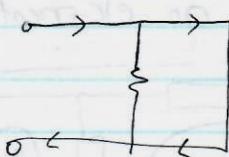

\Rightarrow Short circuit


\hookrightarrow Path of no resistance.

- Ex: //

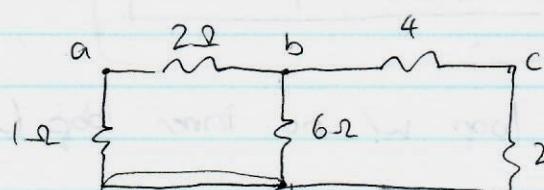

Find R_{eq} between a and d

Redrawings:

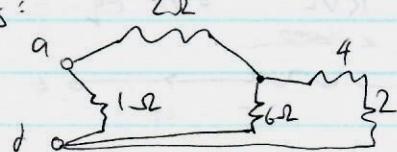


$$\Rightarrow 4-2 \Rightarrow \text{Series.}$$

$$\hookrightarrow \text{parallel wr 6}$$

$$\hookrightarrow \text{series wr 2}$$

Parallel
series wr
1Ω


- Ex: //

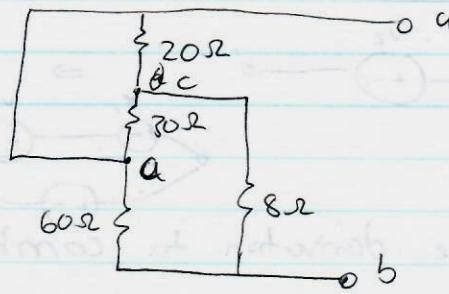

Find R_{eq} between a and b.

Is this a short circuit? No \Rightarrow every path has resistance.

1. Redraw diagram:

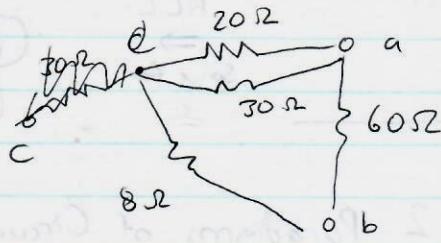

\Leftarrow Key!!

Identify nodes + connect.

Minimize empty wires.


2. Calculate:

$$R_{eq} = \frac{20 \times 30}{20 + 30} = 12 \Omega$$

8Ω in series: 20Ω

$$R_T = \frac{20 \times 60}{20 + 60} = \frac{1200}{80} = \boxed{15 \Omega}$$


CURRENT + VOLTAGE DIVISION

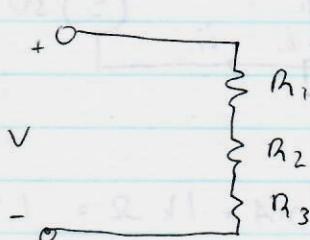

$$V_{R_1} = \frac{R_1}{R_1 + R_2 + R_3} V$$

$$V_{R_2} = \frac{R_2}{R_1 + R_2 + R_3} V$$

Series circuit!

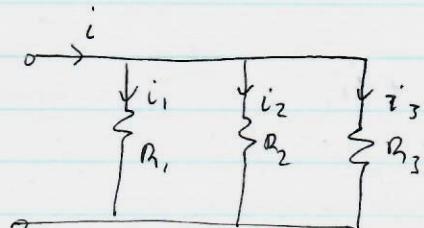

$$i_1 = \frac{R_1}{R_1 + R_2 + R_3} i$$



$$i_2 = \frac{R_2}{R_1 + R_2 + R_3} i$$

Parallel circuit!


Use: when you know all resistor values.

Midway

VOLTAGE + CURRENT SOURCE EQUIVALENCE

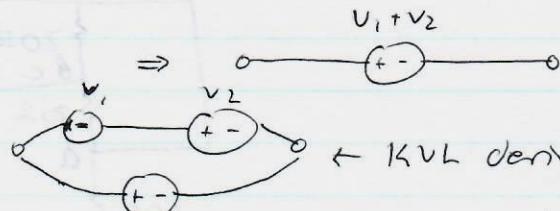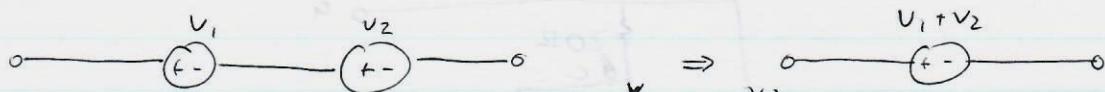

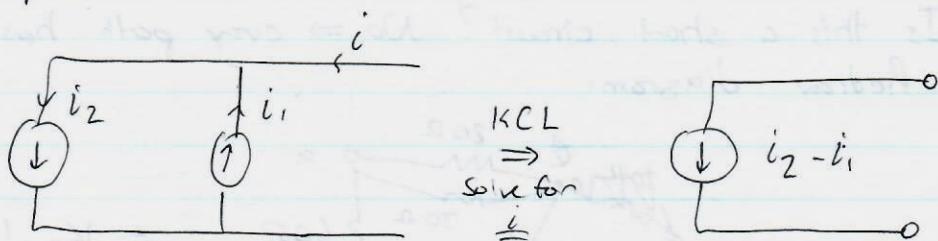Use the same derivation to combine sources in differing polarities.



2 Paradigms of Circuit


KCL, KVL + Ohm's Law

- Requires special attention to passive sign convention

- Ex: //

Circuit Reduction

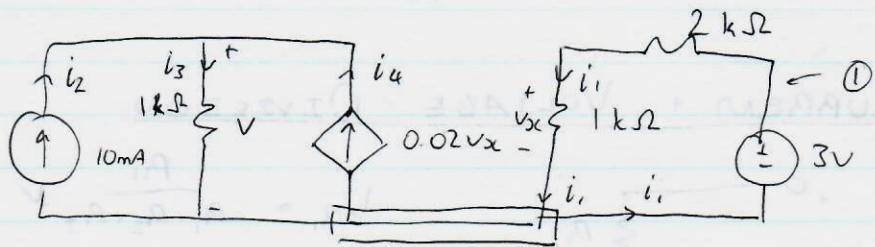- Requires resistor + source equivalence + Ohm's Law



Find v_x :

①: Analyze circuit branch ①

$$R_{T1} = 3 \text{ k}\Omega \quad v_x = 1 \text{ mA} \times 1 \text{ k}\Omega = 1 \text{ V}$$

$$i_1 = 1 \text{ mA}$$

②: KCL on squared node:

$$i_1 + i_3 = i_2 + i_4 + i_x$$


$$i_3 = i_2 + i_4$$

③: Solve for $i_3 + v_x$:

$$i_3 = 10 \text{ mA} + 0.02 \times 1 = 30 \text{ mA}$$

$$v_x = \frac{i_3 \cdot R_x}{30 \text{ V}}$$

NODAL ANALYSIS

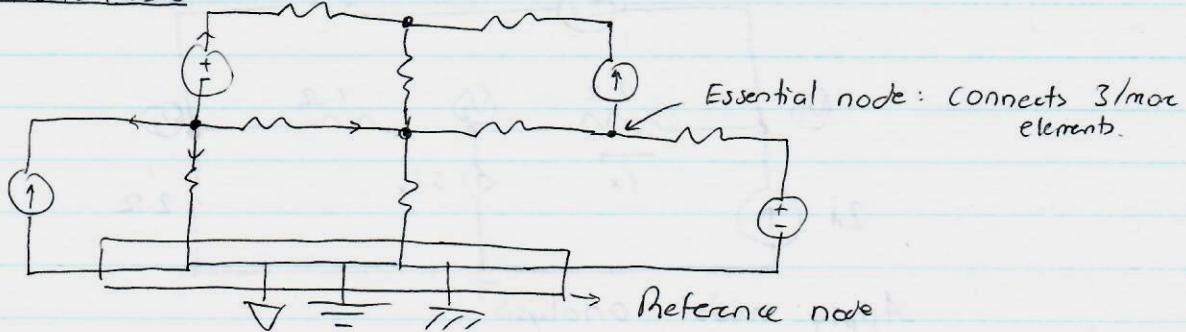


Each essential node has node voltage (voltage drop to ref. node)

General recipe:

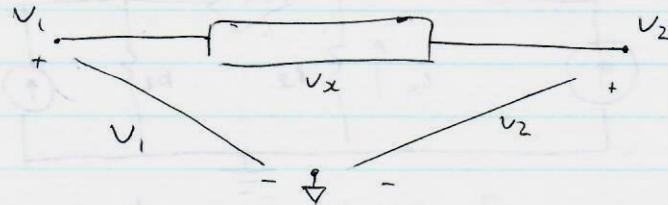1. Define essential + reference nodes + node voltages
2. Assign currents to branches (optional) + make them leave node.
3. Perform KCL on all essential nodes.
4. Express currents in terms of node voltages + resistors (Ohm's Law)
 - ↪ Passive sign convention: don't worry about it.
5. Solve.

Step 4: 3-point rule/ \leftrightarrow voltage source



Performing KVL: $v_x = v_1 - v_2$

$$i_x = \frac{v_1 - v_2}{R}$$

Just take voltage difference across branch + divide by resistor.

If voltage source in branch:


- ① Source is between node + reference.

Define voltage at node = voltage source.

- ② Source is between 2 nodes.

Account for it in 3 point rule
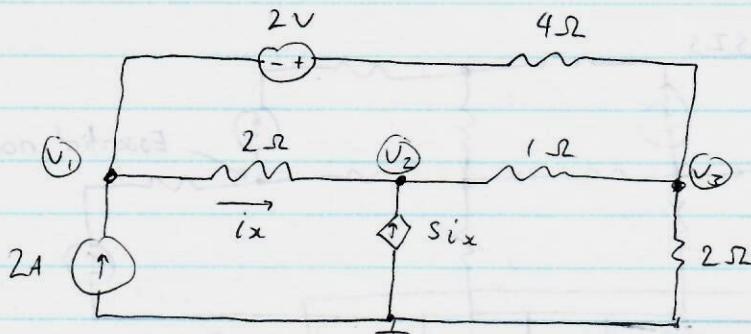
$$v_2 \xrightarrow{R} \text{voltage source} \xrightarrow{R} v_1 \xrightarrow{R} v_x \Rightarrow i_x = \frac{v_2 - v_1 - v_s}{R}$$



Apply nodal analysis:

At node ①:

$$\frac{V_1 + 2 - V_3}{4} + \frac{V_1 - V_2}{2} - 2 = 0 \quad (1)$$


At node ②:

$$\frac{V_2 - V_1}{2} - 5 \left(\frac{V_1 - V_2}{2} \right) + \frac{V_2 - V_3}{1} = 0 \quad (2)$$

At node ③:

$$\frac{V_3 - V_1 - 2}{4} + \frac{V_3 - V_2}{1} + \frac{V_3}{2} = 0 \quad (3)$$

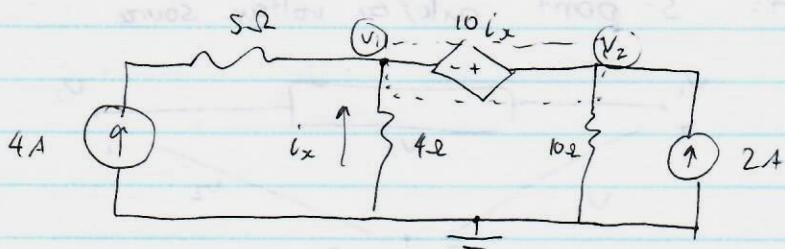Supernode: only a voltage source between two non-reference nodes.




Can be defined anywhere.

1. Make your 2 neighboring nodes + voltage source as 1 node (supernode)
2. Make equations using that supernode:

KCL @ supernode:


$$-4 + \frac{V_1}{4} + \frac{V_2}{10} - 2 = 0$$

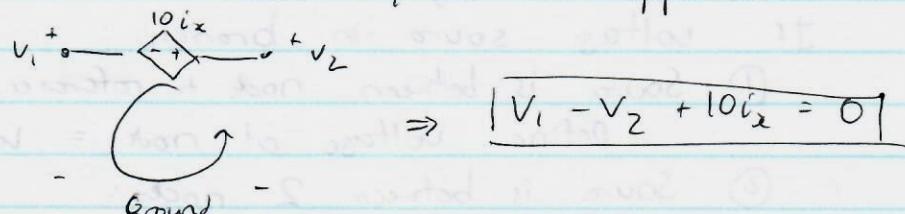3. Use KVL to make equation at supernode:



4. Solve.

MESH ANALYSIS

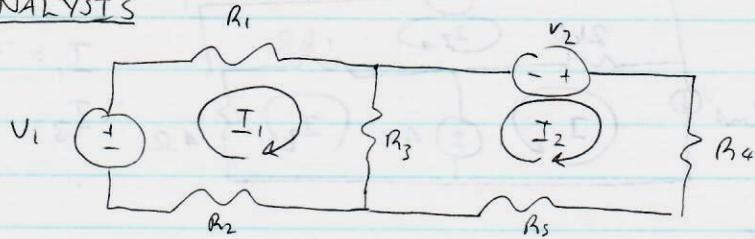

1. Define a mesh current: imaginary current that flows around a mesh
2. Write branch currents in terms of mesh current
 - ↳ What if an element is shared between 2 meshes:
Current: Cur of 1 loop - Cur of other

$$\left. \begin{array}{l} I_1 \\ I_2 \end{array} \right\} \Rightarrow i = I_1 - I_2$$

$$\Rightarrow i = I_2 - I_1$$

3. Perform KVL in each mesh in direction of mesh current
 - Assume every resistor is drop
 - Sources:

Voltage source: contributes to KVL


Current source:

↳ Only in 1 mesh: mesh current = current source

↳ Shared: supermesh

4. Use Ohm's Law + mesh currents to solve for mesh currents.
 - ↳ Express ALL unknowns w/ mesh currents


- Ex: //

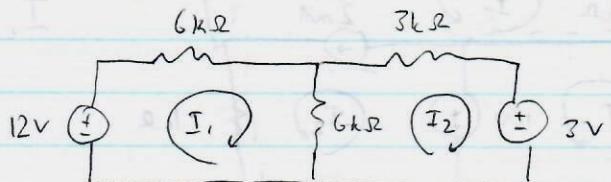

$$\textcircled{1}: -12 + 6I_1 + 6(I_1 - I_2) = 0$$

$$\textcircled{2}: 6(I_2 - I_1) + 3(I_2) + 3 = 0$$

- Ex: //

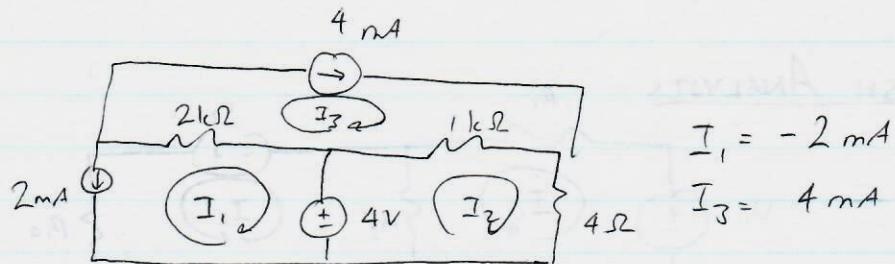

$$I_1 = -2 \text{ mA}$$

$$I_3 = 4 \text{ mA}$$

$$\textcircled{1}: 2(I_1 - I_3) + 4 = 0$$

$$\textcircled{2}: -4 + (I_2 - I_3) + 4I_2 = 0 \Rightarrow \text{This one is needed! } I_2 \text{ is unknown}$$

$$\textcircled{3}: 2(I_3 - I_1) + (I_3 - I_2) = 0$$

Supernodes: current source shared between meshes

1. Create meshes by ignoring branch w/ shared current (supernode)
2. Within the supernode, do KVL w/ original mesh current.
3. Create a equation for shared current source.

$$\leftarrow I_2$$

$$I_A$$


$$I_1$$

I_A is sum in I_1 dir.

$$\therefore I_1 > I_2$$

$$\therefore I_A = I_1 - I_2$$

- Ex: //

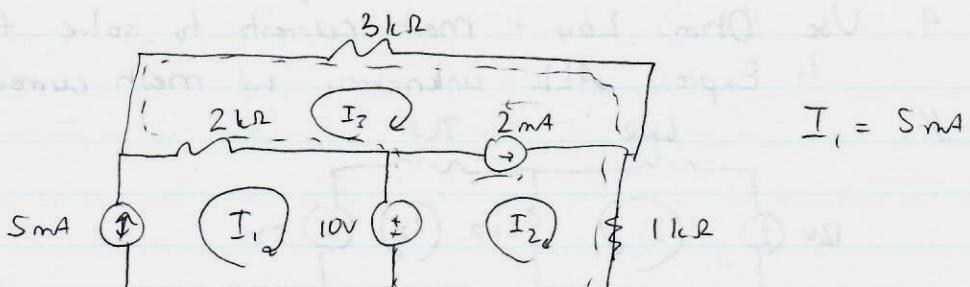

$$I_1 = 5 \text{ mA}$$

$$\textcircled{1}: -10 + 2(I_3 - I_1) + 3I_3 + I_2 = 0$$

$$\textcircled{2}: I_2 - I_3 = 2$$

Nodal vs. Mesh


Nodal:

- Parallel circuits
- Current sources
- Less nodes < meshes

Mesh:

- Series circuits
- Voltage sources
- Less meshes < nodes

LINEARITY

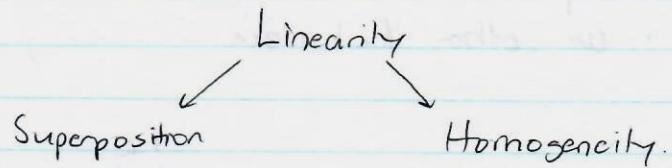

①: Superposition:

Current/voltage across an element = sum of the individual contributions of each indp. source.


1. Turn off voltage/current:

$0V \Rightarrow$ short circuit. $0A \Rightarrow$ open circuit


2. Calculate desired output

3. Add them up.

Ex://

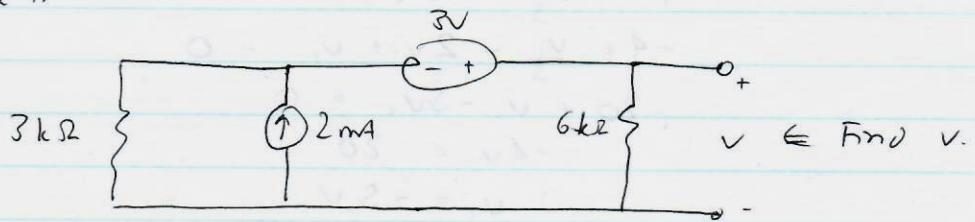


1. Turn off voltage.

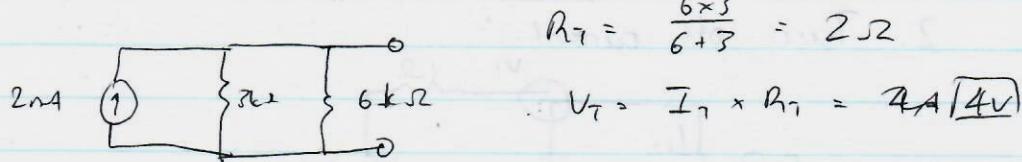

$$R_T = \frac{6 \times 3}{6 + 3} = 2\Omega$$

$$V_T = I_T \times R_T = 2A / 4V$$

2. Turn off current source.

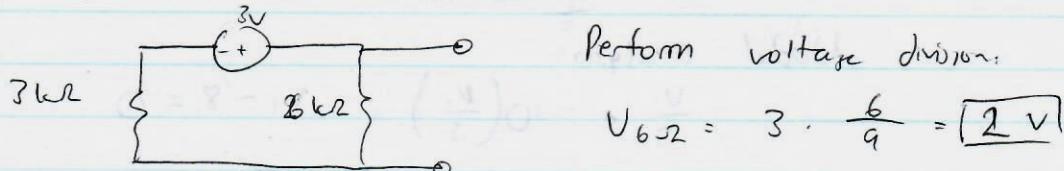

Perform voltage division.

$$V_{6\Omega} = 3 \cdot \frac{6}{9} = 2V$$


3. Total:

$$V_T = V_{2mA} + V_{3V} = 4 + 2 = 6V$$


Hilary

Dealing w/ dependent sources: stick to rules (turning off indep. sources) + use other techniques.

Ex. //

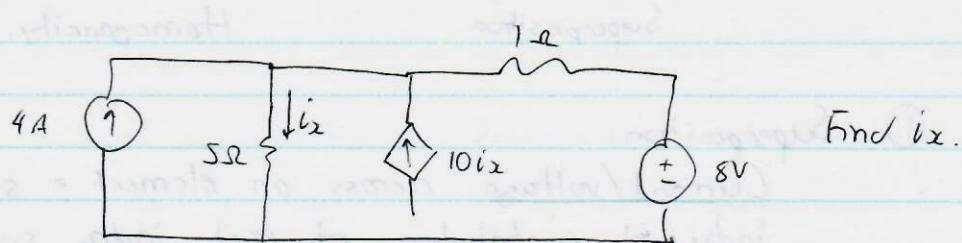

1. Turn off voltage circuit:

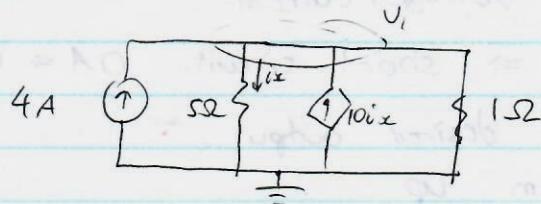

Nodal analysis:

$$-4 + \frac{v_1}{5} - 10\left(\frac{v_1}{5}\right) + v_1 = 0$$

$$-4 + \frac{v_1}{5} - 2v_1 + v_1 = 0$$


$$-20 + v_1 - 5v_1 = 0$$

$$-4v_1 = 20$$

$$v_1 = -5V$$

$$\therefore i_x = -1A$$

2. Turn off current:

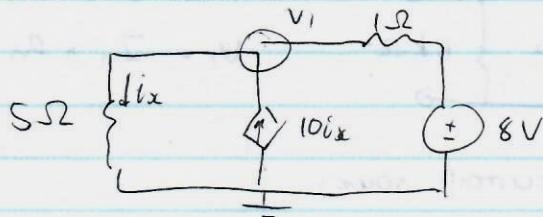

Nodal analysis:

$$\frac{v_1}{5} + -10\left(\frac{v_1}{5}\right) + v_1 - 8 = 0$$

$$\frac{v_1}{5} - 2v_1 + v_1 - 8 = 0$$


$$v_1 - 5v_1 - 40 = 0$$

$$v_1 = -10V$$

$$i_x = -2A$$

3. Total: $i_x = i_x' + i_x'' = -1 - 2 = \boxed{-3A}$


② Homogeneity:

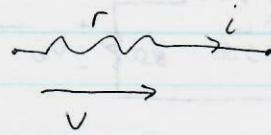

$$\left. \begin{array}{l} \\ \end{array} \right\} 2 \times V \Rightarrow 2 \times i \Rightarrow \text{Ratio constnt}$$

Useful: find ratios between known + unknown part of circuit + solve.

Ex. //

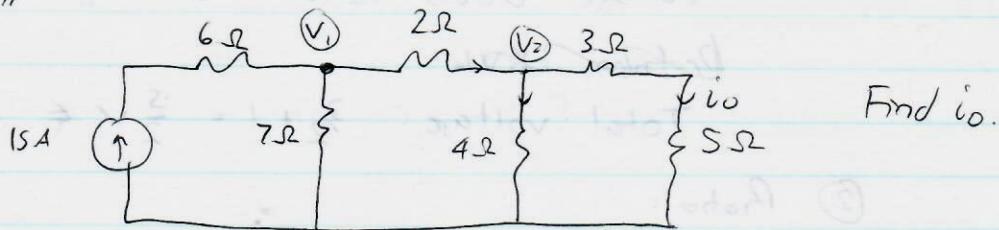

Find i_0 .

①: Assume unknown value $\Rightarrow i_0 = 1A$ (usually put 1)

$$V_2 = 8\Omega \cdot i_0 = 8V$$

$$\text{Current across } 4\Omega = \frac{8}{4} = 2A$$

∴ By KCL, current across 2Ω : 3A

②: Reverse engineer to known value.

$$\frac{V_1 - V_2}{2} = 3 \leftarrow \text{By nodal}$$

$$V_1 = 6 + 8 = 14V$$

$$\text{Current across } 7\Omega: \frac{V_1}{7} = \frac{14V}{7\Omega} = 2A$$

$$\text{By KCL: } \underline{I_s} = 2A + 3A = 5A.$$

③ Ratio:


$$\frac{I_s}{I_0} = \frac{15}{i_0}$$

$$\frac{5}{1} = \frac{15}{i_0}$$

$$\boxed{i_0 = 3A}$$

Hilary

Ex://

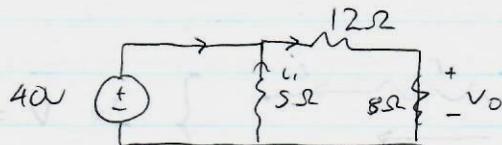

Find v_o via homogeneity

① Assumptions: $v_o = 1 \text{ V}$

$$\text{If } v_o = 1 \text{ V} \Rightarrow I = \frac{V}{R} = \frac{1}{8} \text{ A}$$

$$\text{Voltage across } 12\Omega: V = \frac{1}{8} \times 12 = \frac{3}{2} \text{ V}$$

Rest of the ~~2 KVL~~

$$\text{Total voltage: } \frac{3}{2} + 1 = \frac{5}{2} \text{ V} \leftarrow \text{voltage source}$$

② Ratio:

$$\frac{V_s}{V_o} = \frac{40}{x}$$


$$\frac{5}{2} = \frac{40}{x}$$

$$x = \frac{40 \times 2}{5} = \boxed{16 \text{ V}}$$


SOURCE TRANSFORMATIONS

Convert between voltage sources \leftrightarrow current sources.

ONLY in following combos:

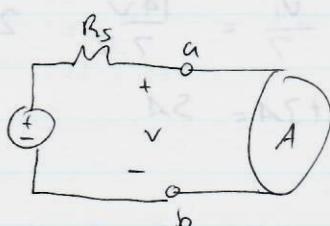

Series voltage

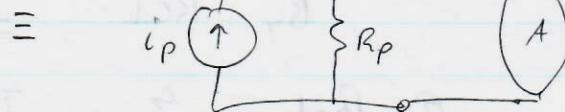


Parallel current

Circuit gets same input
regardless!!

To do this, we will use a combination of short + open circuits \Rightarrow 6000 PROOF TECHNIQUE.

①: Analyzing short circuit current:

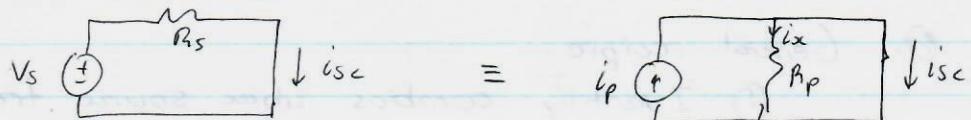

$$i_{sc} = \frac{V_s}{R_s}$$

$$\text{By KCL: } i_p = i_x + i_{sc}$$

$$\text{By shorting: } V_{sc} = 0!$$


$$i_x = \frac{V_{sc}}{R_p} = 0$$

$$i_p = i_{sc}$$

Equations:


$$\frac{V_s}{R_s} = i_p$$

②: Analyze open circuit voltage:

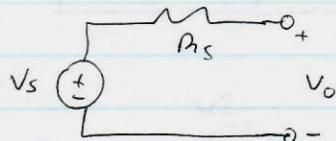

$$V_o = V_s \text{ b/c}$$
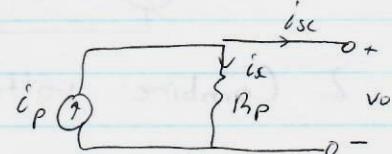
$$i_o = 0 \Rightarrow R_s \text{ has no voltage}$$



$$i_{sc} = 0 \Rightarrow i_x = i_p$$

$$\therefore V_p = R_p \cdot i_p$$

$$\therefore V_o = R_p \cdot i_p$$

$$\text{Equate: } V_s = R_p \cdot i_p$$

③: Equate short + open:

$$V_s = R_s \cdot i_p \text{ from short.}$$

$$V_{s\text{ short}} = V_{s\text{ open}}$$


$$R_s \cdot i_p = R_p \cdot i_p$$

$$\therefore \boxed{R_s = R_p}$$

$$\therefore \boxed{V_s = R_{s/p} \cdot i_p}$$

Use this for source transform.

Help

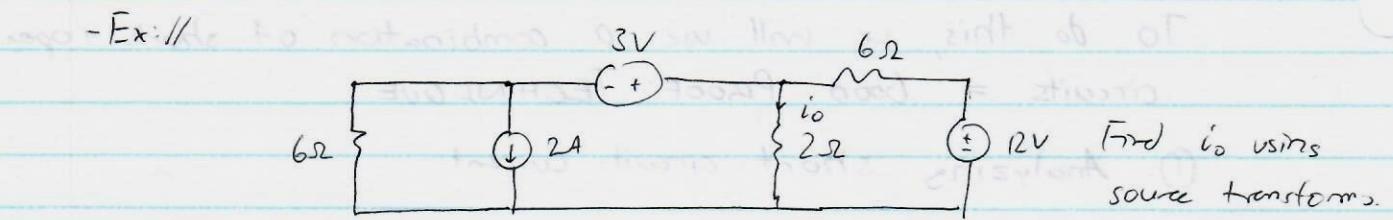


② General recipe:

① Identify combos where source transform can be done


② Transform s.t. sources can be combine + redraw

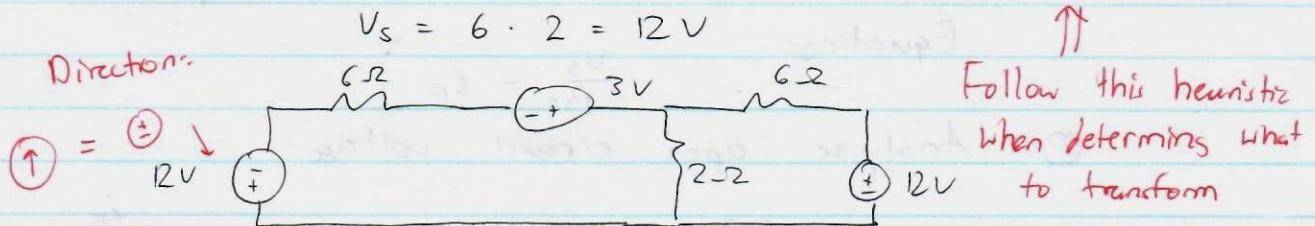1. Convert $6\Omega - 2A$ combo to V:

\hookrightarrow Volt \Rightarrow series
 \hookrightarrow Current \Rightarrow parallel




2. Combine voltages:

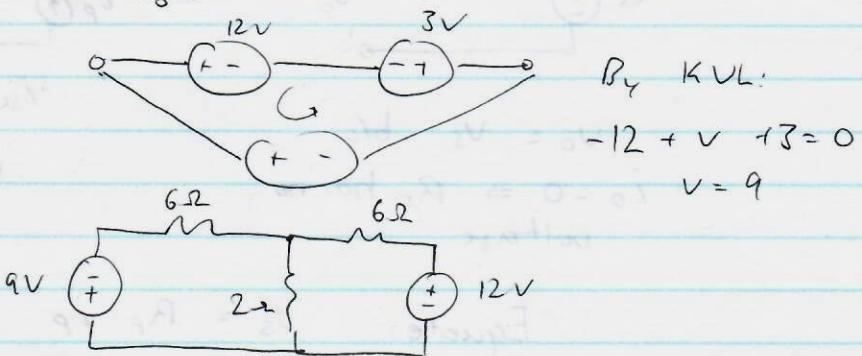


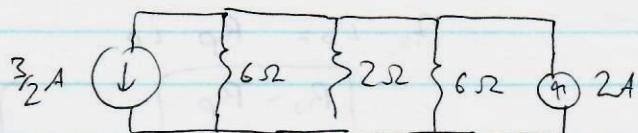3. Creating current sources:

$$9V - 6\Omega: \quad i_p = \frac{9}{6} = \frac{3}{2}A \quad \left\{ \begin{array}{l} 12V - 6\Omega: \\ i_p = \frac{12}{6} = 2A \end{array} \right.$$




4. Combining current:

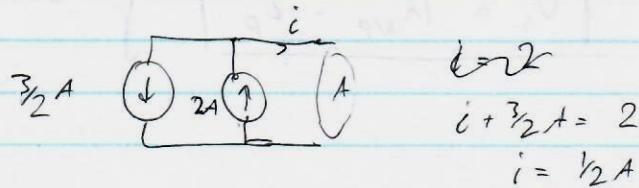

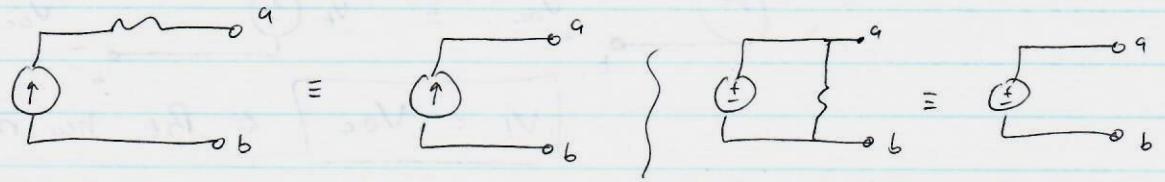
5. Current division

$$i_o = \frac{\frac{1}{2}}{\frac{1}{2} + \frac{1}{3}} \cdot \frac{1}{2} = \frac{\frac{1}{2}}{\frac{5}{6}} \cdot \frac{1}{2} = \underline{0.3A}$$


- If voltage + resistor in parallel or current + resistor in series, ignore the resistor. = no impact on rest of circuit.




Ex: //

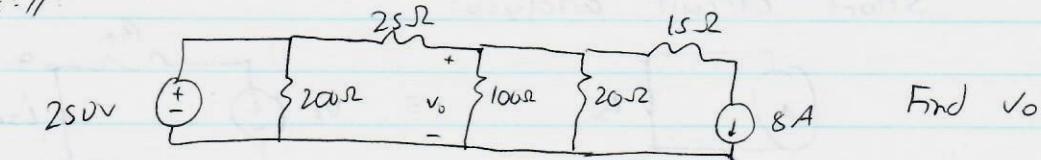

Find V_o

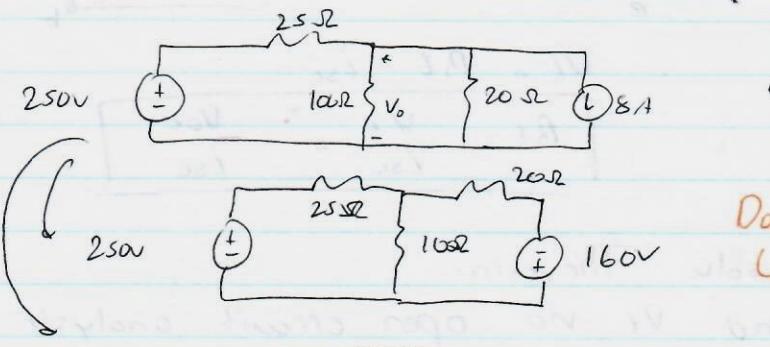

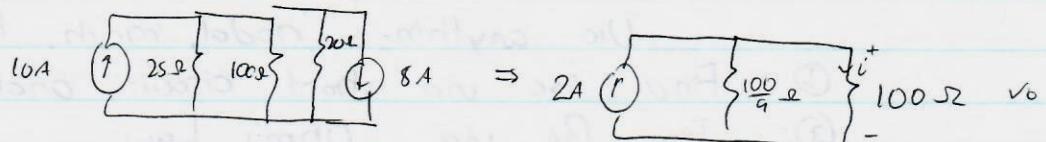Does not work!
↳ Voltage sources not in series! Cannot combin




Current division:

$$i = 2 \cdot \frac{\frac{100}{9}}{\frac{1000}{9}} \quad \left| \begin{array}{l} V_o = 0.2 \times 100 \\ = \boxed{20 \text{ V}} \end{array} \right.$$

- Dependent source: treat it same

THEVENIN EQUIVALENT CIRCUIT

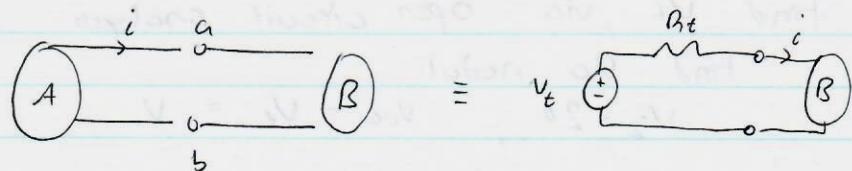


To B, A is just a voltage src + resistor

To find $V_t + R_t \Rightarrow$ Open + short circuit analysis.


Hilary

Open circuit analysis:

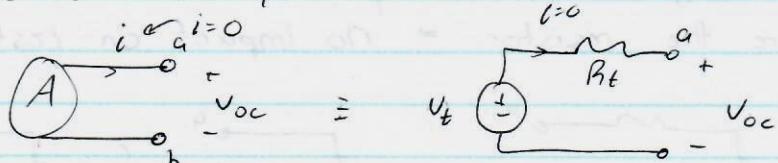

$$\therefore \boxed{V_t = V_{oc}} \leftarrow R_t \text{ has no impact on voltmeter.}$$

Short circuit analysis:

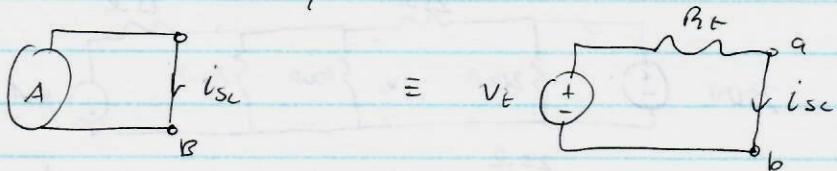

$$V_t = R_t \cdot i_{sc}$$

$$\boxed{R_t = \frac{V_t}{i_{sc}} = \frac{V_{oc}}{i_{sc}}}$$

Steps to solve Thévenin:


①: Find V_t via open circuit analysis:

Use anything: nodal, mesh, KVL, KCL...

②: Find i_{sc} via short circuit analysis:

③: Find R_t via Ohm's Law:

Ex: //

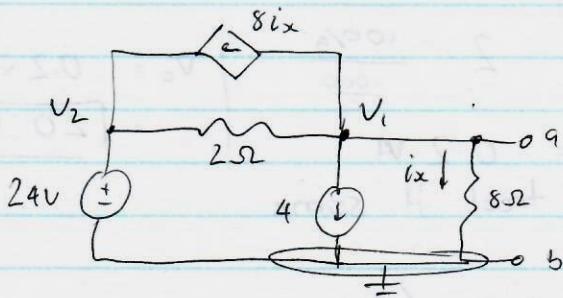

Find Thévenin equivalent between a and b.

①: Find V_t via open circuit analysis:

Find via nodal:


$$V_2 = 24, \quad V_{oc} = V_t = V_1$$

$$\therefore \frac{V_1}{8} + \frac{V_1 - 24}{2} + 4 + V_1 = 0$$

$$\therefore V_1 = 8V$$

$$\therefore \boxed{V_t = 8V}$$

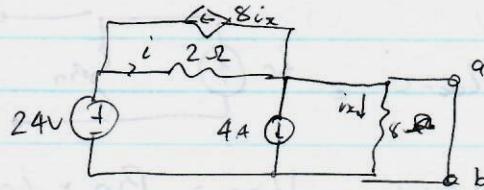②: Finding i_{sc} using short circuit analysis:



From node 1 before:

KCL:

$$i + 8i_x + i_x + i_{sc} = i$$

$$\text{However: } V_{sc} = 0 \Rightarrow i_x = \frac{V}{R} = \frac{0}{8} = 0$$

$$\therefore i_{sc} + 4 = i$$

$$i_{sc} + 4 = \frac{24}{2} \Rightarrow$$

$$\therefore i_{sc} = 8A$$

2Ω // battery

→ Excellent trick!


③: R_T :

$$\therefore R_T = \frac{V_{oc}}{i_{sc}} = 1\Omega$$

Tips:


1. Always find V_t first = easy
2. i_{sc} : Use properties ($sc \Rightarrow V_{sc} = 0$) to eliminate variables.
3. Always note down changed nodes! Shorts cause nodes to change! \Rightarrow Redraw if stuck.

NORTON EQUIVALENT

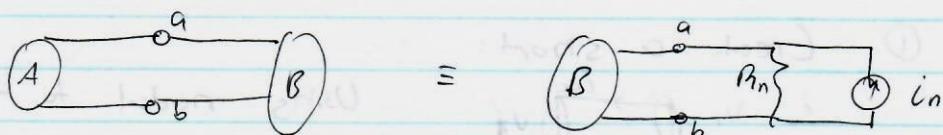

Again, use short + open circuit analysis.


~~Open~~^{Short} circuit analysis:

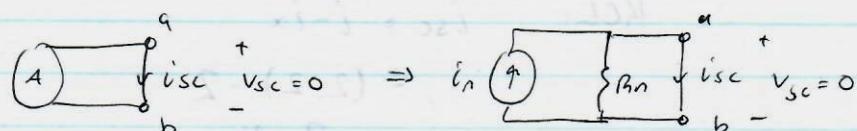

R_n has no effect: $\boxed{i_n = i_{sc}}$

Hurray

Open circuit analysis:

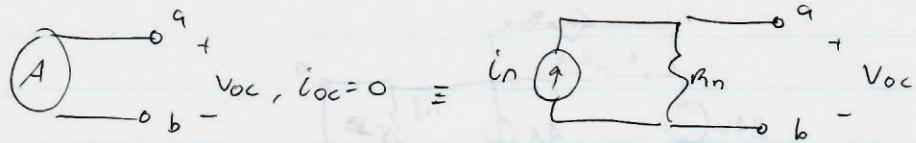

$$\text{By Ohm's Law: } V_{oc} = R_n \times i_n \\ = R_n \times i_{sc}$$

$$\boxed{R_n = \frac{V_{oc}}{i_{sc}}}$$


Comparison between Thévenin + Norton:

$$V_t = V_{oc} \quad i_n = i_{sc} \Rightarrow \text{Easy way to remember:} \\ R_t = \frac{V_{oc}}{i_{sc}} \quad \leftrightarrow \quad R_n = \frac{V_{oc}}{i_{sc}} \quad \text{Choose non-zero components}$$

Steps to solve Norton:


- ①: Short circuit $\rightarrow i_n$
- ②: Open circuit $\rightarrow V_{oc}$
- ③: $R_n \rightarrow$ Ohm's Law.

Ex://

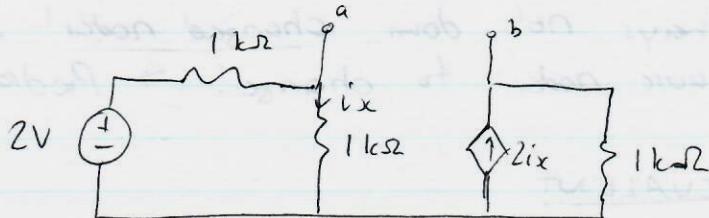

Find Norton equiv. between a and b.

- ① Create a short:

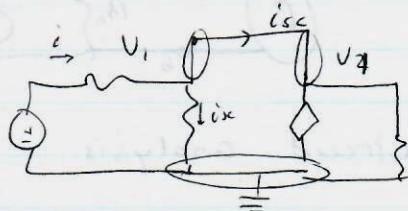

Using nodal to find i_{sc} :

$$\frac{V_1 - 2}{1} + V_1 - 2V_1 + V_1 = 0 \\ V_1 = 0.2V$$

$$\therefore \text{KCL: } i_{sc} = i - i_x$$

$$= (2 - 2) - 2 \\ = -2mA$$

$$\therefore \boxed{i_n = -2mA}$$

① Create open: find V_{OC} :

Nodal analysis:


$$V_1 - 2 + V_1 = 0 \quad -2V_1 + V_2 = 0$$

$$\therefore V_1 = 1V \quad V_2 = 2V$$

$$V_{OC} = -1V \quad (\text{defined from } a \rightarrow b)$$

② Find R_T :
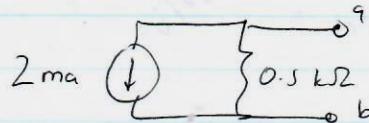
$$R_T = \frac{V_{OC}}{i_{SC}} = \frac{-1V}{-2mA} = 0.5 k\Omega$$




Tips:

- ① Always do short first \rightarrow much easier
↳ Be careful w/ nodes!
- ② Pay attention to direction!

FINDING R_T / R_N TRICKS

① Equivalent resistance: only if all sources are indep.

Ex://

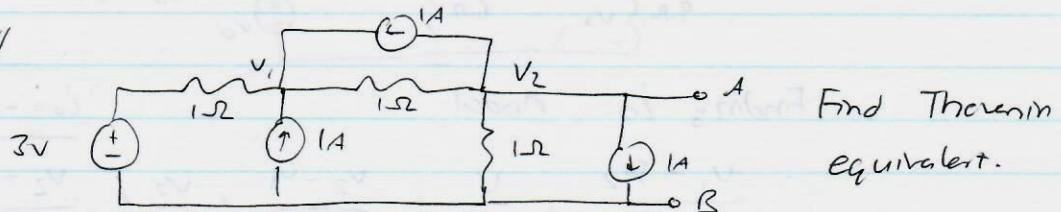

1. Open circuit analysis:

Nodal:


$$①: \frac{V_1 - 3}{1} - 1 - 1 + \frac{V_1 - V_2}{1} = 0$$

$$②: 1 + \frac{V_2 - V_1}{1} + \frac{V_2}{1} + 1 = 0$$

$$V_{OC} = V_2 = \frac{1}{3}V$$

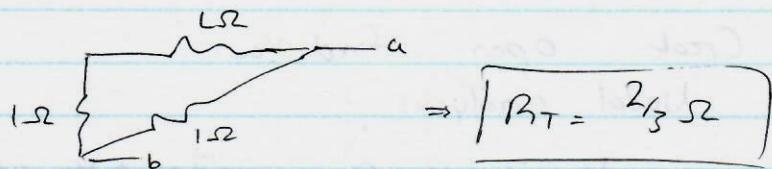2. Short circuit analysis via i_{SC} / equivalent resistance: $\Rightarrow R_T$


- { #1: Turn off all sources
#2: Combine resistors to find R_T



②: Test sources: if dependent sources in circuit


- #1: Find v_{oc} / i_{sc} based on prev. method.
- #2: Turn off all indep. sources
- #3: Insert a voltage/current source: v_o/i_o
- #4: Find current/voltage across element: $i_o/v_o = \frac{I_o}{v_o}$ terms of #3
- #5: $R_{TH} = \frac{v_o}{i_o}$

Ex://

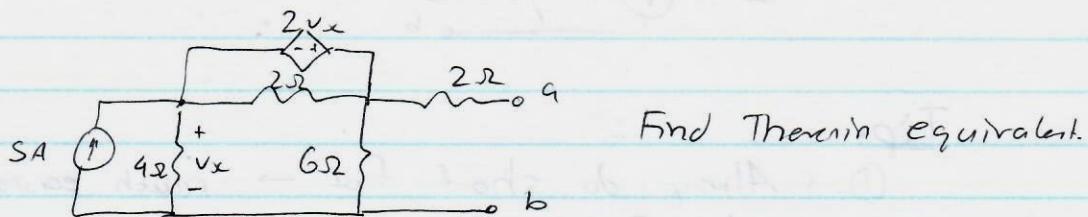

Finding R_{TH} :

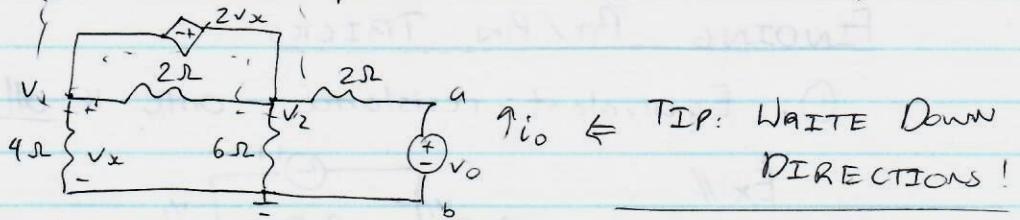Turned off all indep. sources + inserted voltage source v_o :



Finding i_o : nodal:

$$i_o = -i_3$$

$$\frac{v_1 - v_2}{2} + \frac{v_1}{4} + \frac{v_2 - v_1}{2} + \frac{v_2}{6} + \frac{v_2 - v_o}{2} = 0 \quad \text{--- (1)}$$

$$v_1 + 2(v_1) = v_2$$

$$3v_1 = v_2 \quad \text{--- (2)}$$

$$(1): 3v_1 + 2v_2 + 6v_2 - 6v_o = 0$$


$$9v_2 = 6v_o$$

$$v_2 = \frac{2}{3}v_o$$

$$i_o = -\left(\frac{v_2 - v_o}{2}\right) = -\left(-\frac{v_o}{6}\right) = \frac{v_o}{6}$$

$$R_{TH} = \frac{v_o}{i_o} = \underline{6 \Omega}$$

MAXIMUM POWER TRANSFER

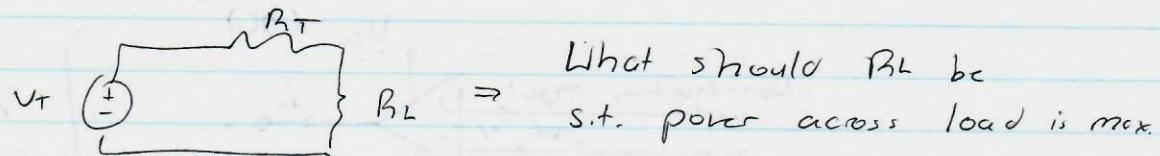

Derivation:

$$P = IV = I^2 R_L = \left(\frac{V_T}{R_T + R_L}\right)^2 \cdot R_L$$


Maximize P w/ respect to R_L .

Solving:

$$\textcircled{1}: R_{L\max} = R_T$$

$$\textcircled{2}: P_{L\max} = \frac{V_T^2}{4R_T}$$

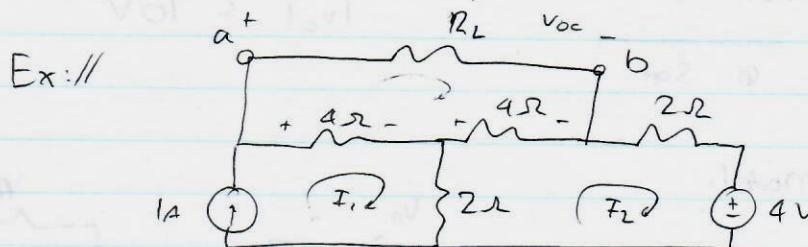To solve max power transfer problem: find Thevenin equivalent w/ respect to R_L .



Find R_L s.t. it absorbs max pow.

#1: Find Thevenin equivalent: mesh analysis.

$$I_1 = 1A$$


$$\textcircled{1}: 2(I_2 - 1) + 4I_2 + 2I_2 + 4 = 0$$

$$I_2 = -\frac{1}{4}A$$

Find $V_{oc} \Rightarrow$ KVL

$$\begin{aligned} V_{oc} &= 4I_1 + 4I_2 \\ &= 4 - 1 \\ &= 3V \end{aligned}$$


Find R_T via equivalent resistors:

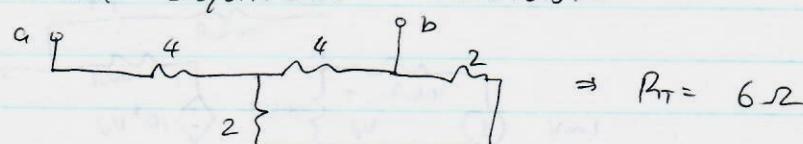

$$\therefore R_L = \underline{6\Omega} \quad P_L = \frac{V_T^2}{4R_T} = \frac{9}{4 \cdot 6} = \underline{\frac{3}{8}W}$$

Hilary


OPERATIONAL AMPLIFIERS

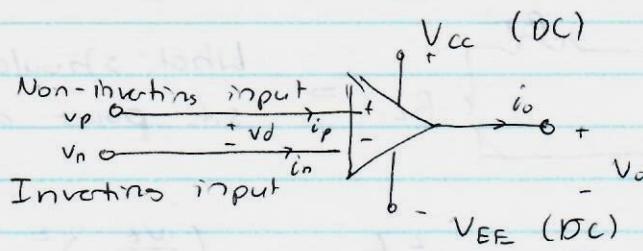

Ability:

- Addition - Intes.
- Subtraction - Diff.
- Amp.

- Characteristics:

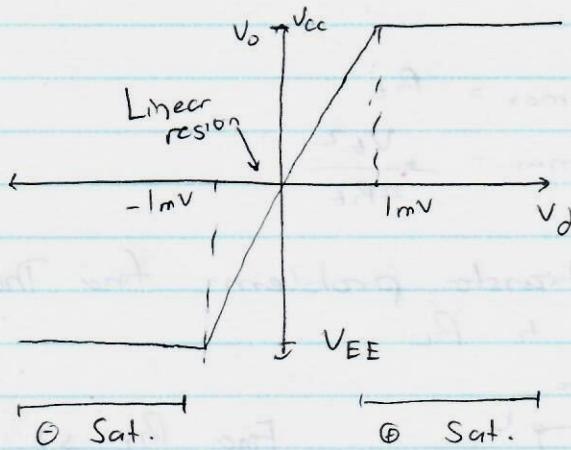

Slope: A

↳ Open-circuit voltage gain ($10^4 - 10^8$)




Analysis in linear region.

$$|v_d| \leq 1\text{mV}$$


$$|v_o| \leq 10\text{V}$$

- 2 models


1. Linear model:

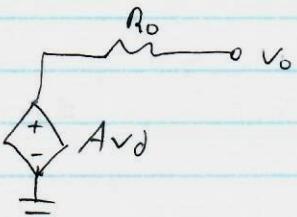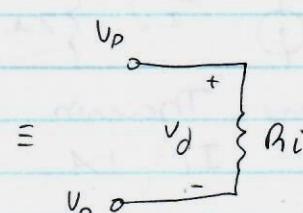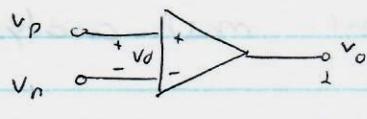

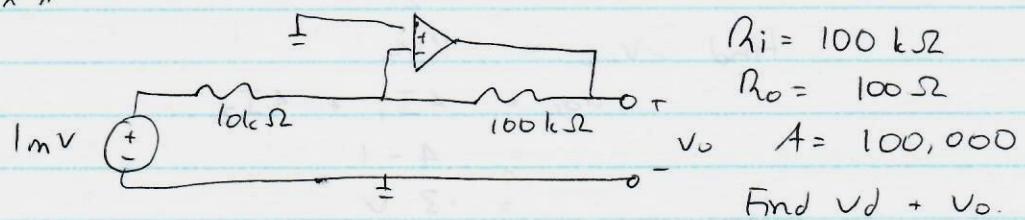To solve q., simply replace op-amp w/ circuit.
- Ex://



Using linear model approximation:

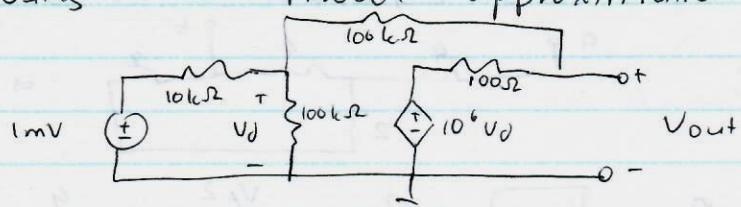


Using nodal:

$$\frac{V_1 - 10^{-3}}{10 \times 10^3} + \frac{V_1}{100 \times 10^3} + \frac{V_1 - V_0}{100 \times 10^3} = 0 \quad -\textcircled{1}$$

Works really well
if Nodal + op-amp

$$\frac{V_0 - V_1}{100 \times 10^3} + \frac{V_0 - 10^6 V_1}{100} = 0 \quad -\textcircled{2}$$

2. Ideal model:

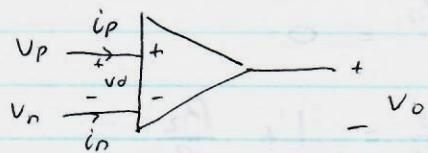


$$\textcircled{1}: V_p = V_n \text{ (roughly)}$$

$$\textcircled{2}: i_p = i_n = 0.$$

Extremely versatile. Use nodal w/ ideal model by identifying $V_p + V_n$.

- Inverting amplifier:

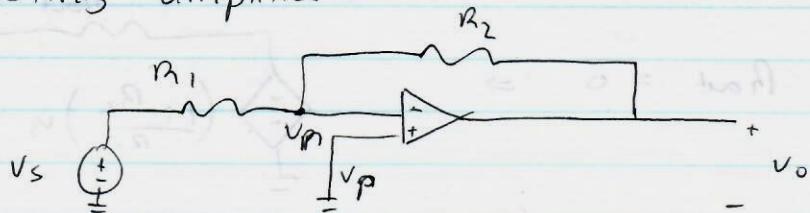

Analysing via ideal model:

① Identity $V_p + V_n$

$$V_p = 0 \Rightarrow V_p = 0.$$

②: KCL on nodes (only on input):

$$\frac{V_n - V_s}{R_1} + \frac{V_n - V_0}{R_2} + i_n = 0$$


$$-\frac{V_s}{R_1} - \frac{V_0}{R_2} = 0$$

$$\therefore \boxed{V_0 = -\frac{R_2}{R_1} V_s}$$

6V (closed circuit gain)

$R_{in} = R_1$, $R_{out} = 0$ (resistance seen by V_s + V_0 respectively)

- Non-inverting amplifier:

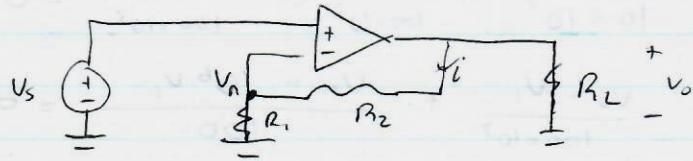

$$V_p = V_n = V_s$$

KCL at V_n :


$$\frac{V_n}{R_1} + \frac{V_n - V_o}{R_2} = 0$$

$$\therefore G_v = \frac{V_o}{V_s} = 1 + \frac{R_2}{R_1}$$

• Input resistance:

$$R_{in} = \frac{V_s}{i_s} \Rightarrow \lim_{i_s \rightarrow 0} R_{in} = \infty$$

$$R_{out} = 0 \Rightarrow$$

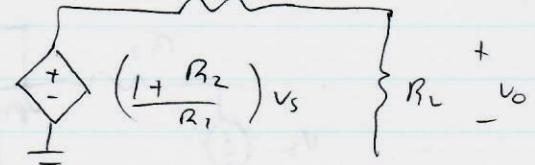

$$\text{Since } V_o = \left(1 + \frac{R_2}{R_1}\right) V_s \Rightarrow R_{out} = 0$$

• Output current:


$$i_o = i_L + i = \frac{V_o}{R_L} + \frac{V_o - V_s}{R_2}$$

$$= \frac{V_o}{R_L} + \frac{V_o}{R_1 + R_2}$$

$$= \frac{V_o}{R_L} + \frac{V_s}{R_1}$$


R_1 is in series w/ R_2 .

- Adder amplifier:

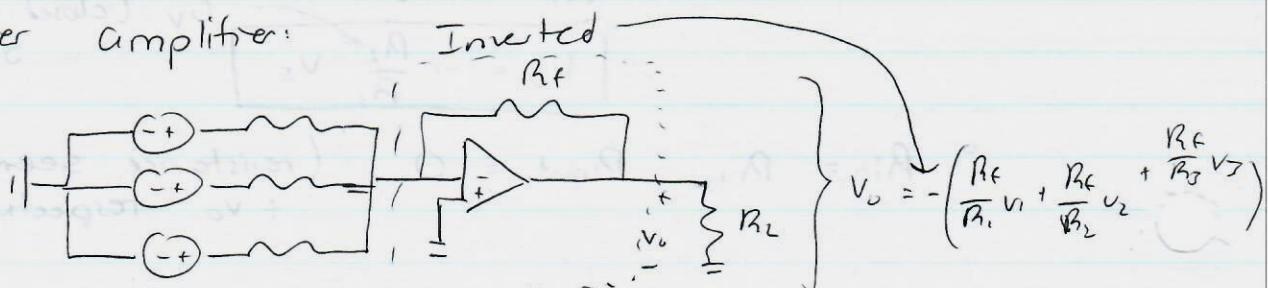

NOTE: Terminal from output $\rightarrow \Theta$. Want to prevent \oplus saturation


- Difference amplifier:

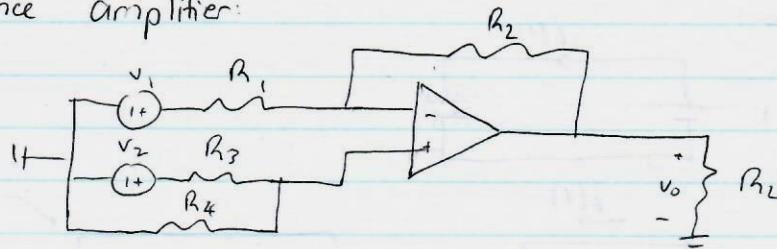

$$v_o = \frac{R_2}{R_1} \left[\left(\frac{R_1/R_2 + 1}{R_3/R_4 + 1} \right) v_2 - v_1 \right]$$

$$\text{For } \frac{R_1}{R_2} = \frac{R_3}{R_4} \Rightarrow v_o = \frac{R_2}{R_1} (v_2 - v_1)$$

- Ex: // Chained amplifier

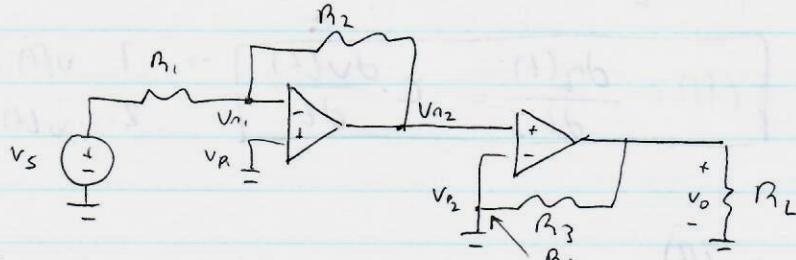

①: $v_n + v_p$ for each amp:

②: Apply KCL @ input:

$$\frac{v_{n1} - v_s}{R_1} + \frac{v_{n1} - v_{n2}}{R_2} = 0, \quad v_{p1} = v_{n1} = 0$$

$$v_{n2} = -\frac{R_2}{R_1} v_s \Rightarrow \text{Inverting amplifier}$$

③: Apply KCL @ 2nd input:



$$\frac{v_{p2}}{R_4} + \frac{v_{p2} - v_o}{R_3} = 0 \quad v_{p2} = v_{n2} = -\frac{R_2}{R_1} v_s$$

$$v_o = \left(1 + \frac{R_3}{R_4} \right) \left(-\frac{R_2}{R_1} \right) v_s$$

We multiplied effect on inverting + non-inverting amplifier.

Identify individual op amps → find individual output voltages, which are input voltages of next op amp → continue forward.

CAPACITORS

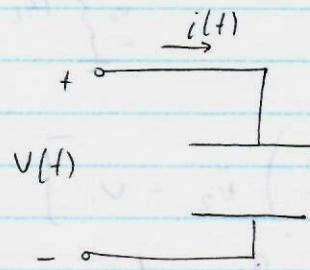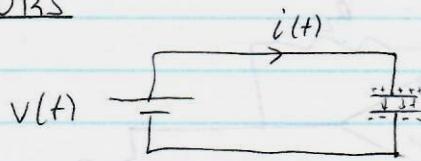

$$C = \frac{q(t)}{V(t)}$$

Measured in Farads

(C is property of capacitor)



To put this in terms of current:

$$q(t) = C \cdot V(t)$$

$$i(t) = \frac{dq(t)}{dt} = C \cdot \frac{dV(t)}{dt}$$

- 1. $V(t)$ is constant $\rightarrow i = 0$
- 2. $V(t)$ is continuous

- Ex: //

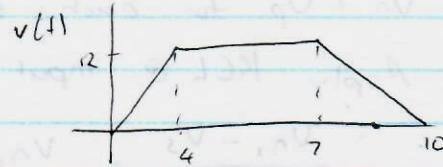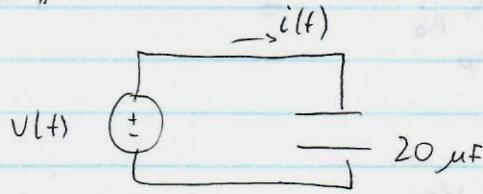

Find $i(t)$.

From $0 \leq t \leq 4$:

$$i(t) = C \cdot \frac{dV(t)}{dt} = 20 \times 10^{-6} \cdot 3 = 60 \text{ mA}$$

From $4 \leq t \leq 7$:

$$i(t) = C \cdot \frac{dV(t)}{dt} = 0 \text{ A}$$

From $7 \leq t \leq 10$:

$$i(t) = C \cdot \frac{dV(t)}{dt} = 20 \times 10^{-6} \cdot -4 = -80 \times 10^{-6} \text{ A}$$

- Finding voltage from capacitors:

$$i(t) = C \cdot \frac{dV(t)}{dt}$$

$$dV(t) = \frac{1}{C} \cdot i(t) dt$$

$$\int dV(t) = \int \frac{1}{C} \cdot i(t) dt$$

$$\begin{aligned} V(t) - V(t_0) &= \frac{1}{C} \int_{t_0}^t i(\tau) d\tau \\ \therefore V(t) &= V(t_0) + \frac{1}{C} \int_{t_0}^t i(\tau) d\tau \end{aligned}$$

- Power + energy:

$$P(t) = v(t) \cdot i(t) \\ = v(t) \cdot C \cdot \frac{dv}{dt}$$

$$\frac{d\omega(t)}{dt} = v(t) \cdot C \cdot \frac{dv}{dt}$$

$$d\omega(t) = Cv(t) dv \\ \int_{t_1}^{t_2} d\omega(t) = \int_{v(t_1)}^{v(t_2)} Cv(t) dv$$

$$\omega(t_2) - \omega(t_1) = C \cdot \frac{v^2(t_2) - v^2(t_1)}{2}$$


Take $t_1 = -\infty$, $v(t_1) = 0$

$$\therefore \boxed{\int \omega = \frac{C \cdot v^2(t)}{2}} \Rightarrow \text{Energy stored in capacitor electric field}$$

Be able from graphs

• Recognize that v^2 on $v(t) =$ lines \rightarrow quadratics.

INDUCTORS

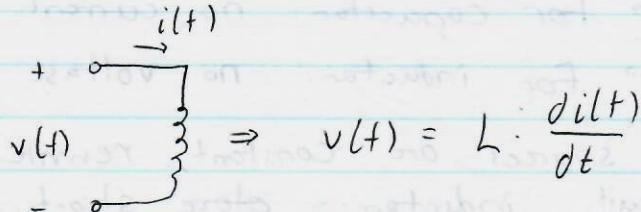

$$L \Rightarrow \text{inductance } (H = \frac{V \cdot S}{A})$$

Formulas for inductors v. similar to capacitors:

$$V \leftrightarrow i \quad C \leftrightarrow L$$

$$i(t) = i(t_0) + \frac{1}{L} \int_{t_0}^t v(\tau) d\tau \quad \text{①}$$

$$W = \frac{1}{2} L (i^2(t_2) - i^2(t_1))$$

- Current follows passive sign convention + must be continuous


①: Set $i_0 = \text{prev } i$ (limits one-sided) \Leftarrow continuity requirement.

②: Use integrals on next stage to get formula

③: Repeat

	Capacitors	Inductors
$v(t)$	Continuous	Stepwise
$i(t)$	Stepwise	Continuous

SOLVING LC CIRCUITS

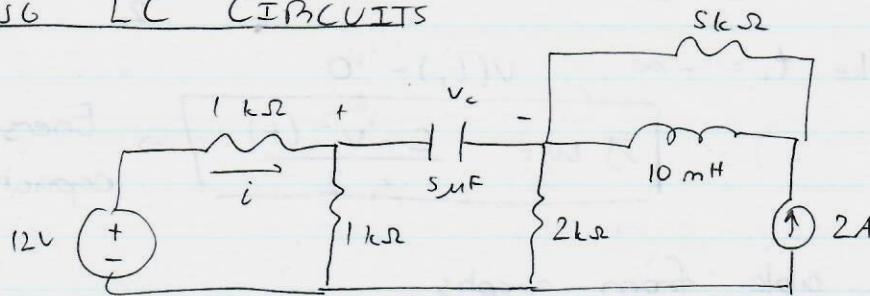


Note that all currents + voltages are constant!

↳ For capacitor: no current ($\frac{dv}{dt} = 0$)

↳ For inductor: no voltage ($\frac{di}{dt} = 0$)

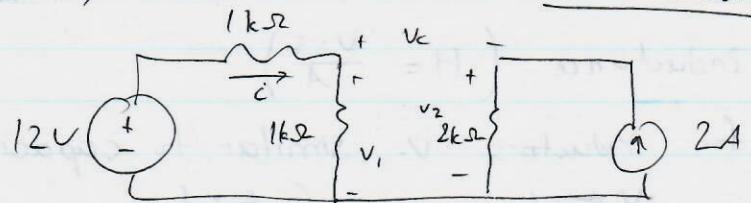① If sources are constant, rewrite w/ capacitors = open circuit, inductors = close short circuits.




②: Solve for current/voltage running through:


$$\therefore i = 6 \text{ mA}$$

$$v_C = v_1 - v_2 = 2 \text{ V}$$

EQUIVALENT CAPACITORS

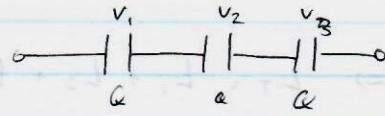

Q is same: induction

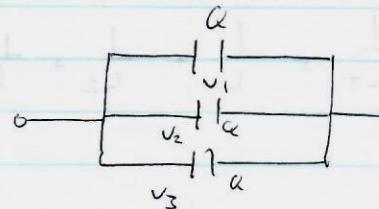

V is same: parallel laws

$$V_T = V_1 + V_2 + V_3$$

$$\frac{Q_T}{C_T} = \frac{Q_1}{C_1} + \frac{Q_2}{C_2} + \frac{Q_3}{C_3}$$

$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$Q_T = Q_1 + Q_2 + Q_3$$


$$C_T V_T = C_1 V_1 + C_2 V_2 + C_3 V_3$$

$$C_T = C_1 + C_2 + C_3$$

Tips for solving capacitor proofs:

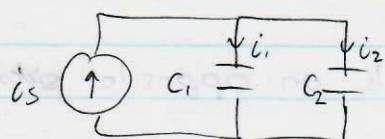1. Recognize Q is same in all capacitors in series.
2. Recognize Q is summed in parallel.
3. Try to put variables in terms of each other via KVL, KCL, etc.

Ex:// Show $i_1 = \frac{C_1}{C_1 + C_2} i_S$ and $i_2 = \frac{C_2}{C_1 + C_2} i_S$



Don't mess w/ equivalent!

$$\textcircled{1}: i_S = i_1 + i_2 \Rightarrow Q_S = Q_1 + Q_2$$

$$\textcircled{2}: V_1 = V_2$$

From \textcircled{2} + using capacitance formula:

$$\frac{Q_1}{Q_1} = \frac{Q_2}{C_2}$$

Using \textcircled{1}:

$$\frac{Q_1}{C_1} = \frac{Q_S}{C_2} - \frac{Q_1}{C_2}$$

$$Q_1 \left(\frac{1}{C_1} + \frac{1}{C_2} \right) = \frac{1}{C_2} Q_S$$


$$Q_1 = \frac{1}{C_2} \cdot \frac{C_1 C_2}{C_1 + C_2} Q_S$$

$$I_1 = \frac{C_1}{C_1 + C_2} Q_S$$

Hilary

EQUIVALENT INDUCTORS


Mimic resistors!

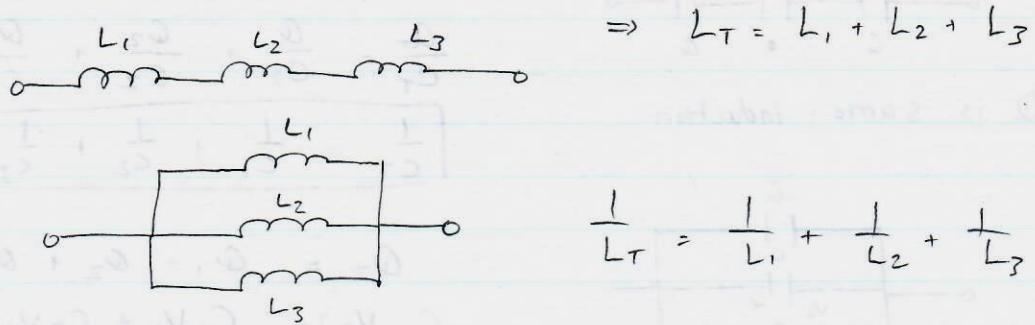

TRANSIENT ANALYSIS

Constant current + voltage \rightarrow time-based V, I

①: Discharge of RC circuit

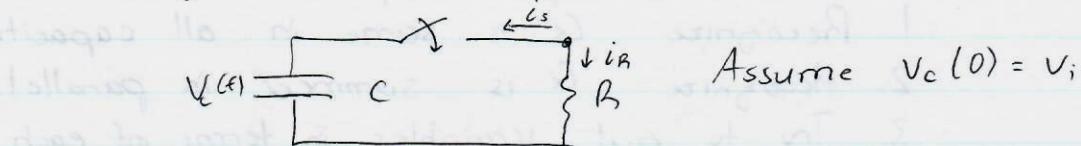

We want to find $V_C(t)$ for $t \geq 0$:

$$i_s + i_R = 0 \quad \leftarrow \text{Want to look at dissipation, so need } i_R$$

$$C \cdot \frac{dV_C(t)}{dt} + \frac{V_C(t)}{R} = 0$$

To solve DE, put differentials on opposite sides + integrate.

$$\frac{dV_C(t)}{V_C(t)} = -\frac{dt}{RC}$$


$$\int_{V(0)}^{V(t)} \frac{dV_C(t)}{V_C(t)} = \int_0^t -\frac{dt}{RC}$$

$$\ln |V_C(t)| \Big|_{V_i}^{V(t)} = -\frac{t}{RC}$$

$$\ln \left(\frac{V(t)}{V_i} \right) = -\frac{t}{RC}$$

$$\boxed{V(t) = V_i e^{-t/RC}}$$
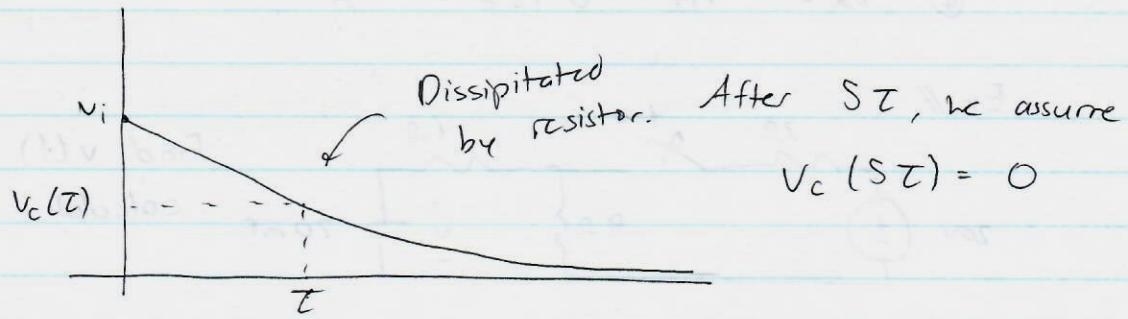
$$\text{Time constant: } \tau = R_C \Rightarrow V(t) = V_i e^{-t/\tau}$$



$\tau \downarrow \rightarrow$ reach steady state faster

$$i_R = \frac{V(t)}{R} = \frac{V_i}{R} e^{-t/\tau}$$

$$\text{Power} = V(t) \cdot i(t) = \frac{V_i^2}{R} e^{-2t/\tau}$$


$$\begin{aligned} \text{Energy: } E(t) &= \int_0^t p(\lambda) d\lambda = \int_0^t \frac{V_i^2}{R} e^{-2\lambda/\tau} d\lambda \\ &= \left[-\frac{\tau V_i^2}{2R} e^{-2\lambda/\tau} \right]_0^t \\ &= \frac{1}{2} C V_i^2 (1 - e^{-2t/\tau}) \end{aligned}$$

W// energy: $t \rightarrow \infty, E(t) = \frac{1}{2} C V_i^2 \Rightarrow \text{Energy dissipated by resistor} = \text{initial energy}$

Tips:

1. Find $V(0)$ ASAP + τ
2. $R = R_{TH}$
3. If $v(t)$ and $i(t)$ given, use it w/ τ to find $R+C$. $R = \frac{V(t)}{i(t)}$
 $E = \frac{1}{2} C (V(t))^2$!

- Ex: //

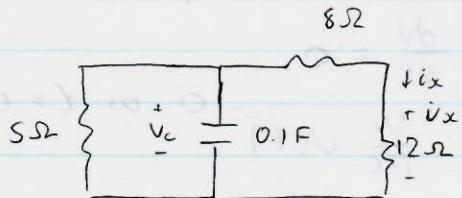

Find V_C, V_x, i_x at $t > 0$
if $V(0) = 15 \text{ V}$.

①: Finding τ by doing R_{TH}

$$4\Omega \left\{ \frac{1}{0.1F} \right\} \Rightarrow \tau = RC = 0.4$$


②: V_C : $V_C(t) = 15 e^{-t/0.4}$

Hilary

$$\textcircled{3}: V_x = V_T \cdot \frac{12}{12+8} = 9e^{-2.5t} \text{ V} \quad (\text{voltage division on series})$$

$$\textcircled{4}: i_x = \frac{V_x}{12} = 0.75e^{-2.5t} \text{ A}$$

- Ex://

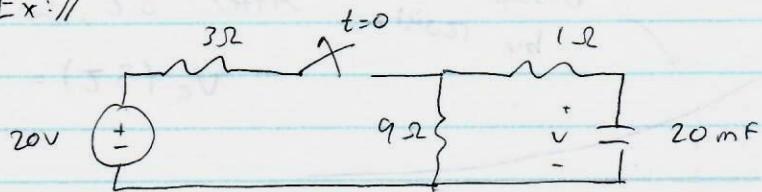

Find $v(t)$ for $t \geq 0$ and calculate initial energy.

Note that V_i is simply found via normal techniques.
When switch is opened, indep. source has no impact.

①: Find V_i :

$$V_i = \frac{9}{3+9} \cdot 20 = 15 \text{ V} \quad \text{Capacitor acts as open!}$$

②: Find T :

$$T = 10 \cdot 20 \times 10^{-3} = 0.2 \text{ s}$$


③: $v(t)$:

$$v(t) = 15e^{-t/0.2} \text{ V}$$

④: Initial energy:

$$E(t) = \frac{1}{2} CV(0)^2 = \frac{1}{2} (20 \times 10^{-3}) (15)^2 = 2.25 \text{ J}$$

②: Charging an RC circuit

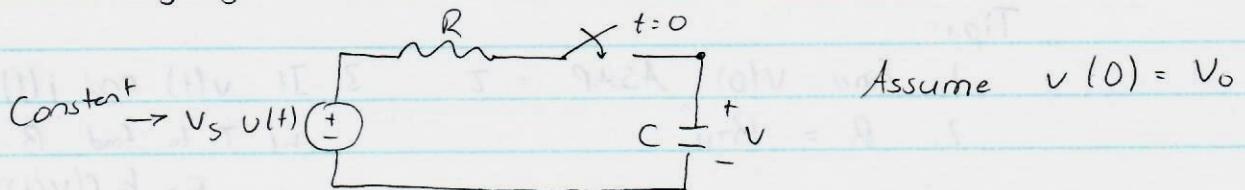

Finding $v(t)$ by doing KCL on top right node:

$$\frac{V - v(t)}{R} + C \frac{dv}{dt} = 0$$

$$\frac{dv}{dt} + \frac{V}{RC} = \frac{V_s}{RC} e^{V_s t} \quad 0 \text{ as } t > 0$$

$$\frac{dv}{V - V_s} = - \frac{dt}{RC}$$

Doing integration:


$$\ln(V - V_s) \Big|_{V(0)}^{V(t)} = -\frac{t}{RC} \Big|_0^t$$

$$\ln \left(\frac{V - V_s}{V_0 - V_s} \right) = -\frac{t}{RC}$$

Complete response. \rightarrow $V(t) = V_s + (V_0 - V_s)e^{-t/\tau}$ $\Rightarrow \tau = RC$

$$V(t) = \begin{cases} 0/V_0 & t=0 \\ V_s(1-e^{-t/\tau}) / V_s + (V_0 - V_s)e^{-t/\tau} & t>0 \end{cases}$$

Uncharged cap. initial

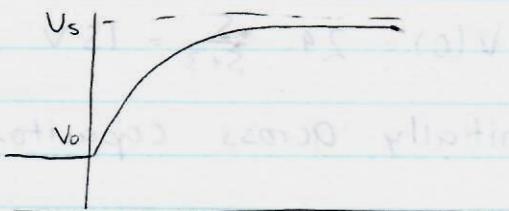

\Rightarrow Graph of step response / complete response.

Current:

$$i(t) = C \cdot \frac{dV}{dt} = C \cdot \left(\frac{V_s e^{-t/\tau}}{\tau} \right) = \frac{C}{\tau} V_s e^{-t/\tau}$$

OR: $i(t) = \frac{V_s e^{-t/\tau}}{R}$

Easier way of analyzing step response:

①: Complete response = natural response (stored) + forced response (input)

$$\therefore V = V_n + V_f$$

$$V_n = V_0 e^{-t/\tau} \quad (\text{from discharge})$$

$$V_f = V_s (1 - e)^{-t/\tau} \quad (\text{from charging})$$

②: Complete response = transient response + steady-state response.

$$V = V_t + V_{ss}$$


$$V_t = (V_0 - V_s) e^{-t/\tau}, \quad V_{ss} = V_s$$

Generally: $V(t) = V(\infty) + (V(0) - V(\infty)) e^{-t/\tau}$ Hilary

If time delay:

$$v(t) = v(\infty) + [v(t_0) - v(\infty)] e^{-\frac{t-t_0}{\tau}}$$

-Ex://

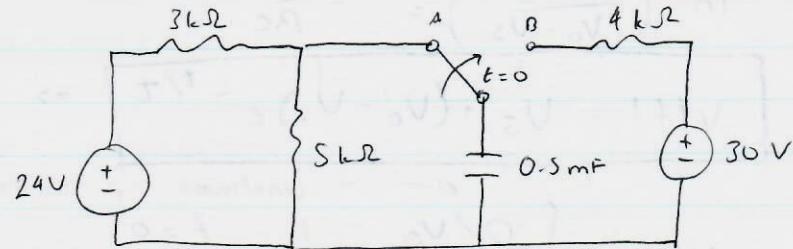

Determine $v(t)$
for $t=1, 4$ s.

①: $v(0)$:

Voltage division across $5\text{k}\Omega$:

$$v_{5\text{k}\Omega} = v(0) = 24 \cdot \frac{5}{5+3} = 15\text{V}$$

∴ 15V initially across capacitor.

②: Switch moves:


$$\tau = R \cdot C = 4\text{k}\Omega \cdot 0.5\text{mF} = 2\text{s}$$

$$v(\infty) = 30\text{V}$$

$$\therefore v(t) = 30 + (15 - 30) e^{-\frac{t}{2}}$$

$$\therefore v(1) = 30 - 15 e^{-\frac{1}{2}} = 20.9\text{V}, \quad v(4) = 27.47\text{V}$$

-Ex://

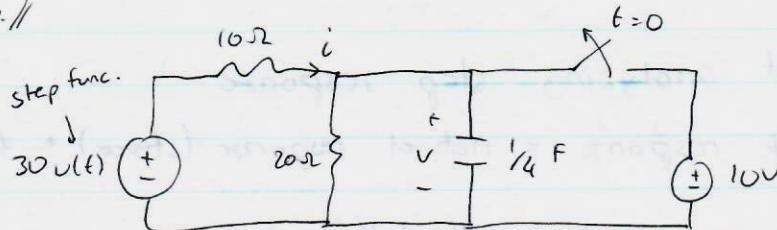

Find $i + v$ for
all time.


$t < 0$:

$$30 \quad v(t) = \begin{cases} 0 & \text{for } t < 0 \\ 30 & \text{for } t \geq 0 \end{cases}$$

All components in parallel:

$$v_0 = 10\text{V}, \quad i = -\frac{V}{R} = -1\text{A}$$

$t > 0$:

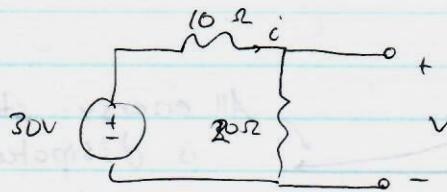

$$T = R_{TH} \cdot C = \cancel{30} \frac{1}{4} F \quad 10/20 - \cancel{1/4} F = \frac{20}{3} \cdot \frac{1}{4} = \frac{5}{3} s$$

$$V(\infty) = \cancel{30V} : 30 \cdot \frac{20}{30} = 20V$$

$$\therefore V(t) = \cancel{30} + \left(10 - \cancel{30}\right) e^{-\frac{3t}{5}}$$

Common mistake!
Need voltage
for capacitor NOT
source.

$$i = \frac{V}{20} + C \frac{dV}{dt} = (1 + e^{-0.6t}) A$$

↑
current on
20Ω res.

$$i(t) = \begin{cases} -1 & t < 0 \\ 1 + e^{-0.6t} & t \geq 0 \end{cases}, \quad V(t) = \begin{cases} 10 & t < 0 \\ 20 - 10e^{-0.6t} & t \geq 0 \end{cases}$$

How to solve BC problems:

① Analyze $t < 0$ for $V(t)$, $i(t)$

↳ Keep in mind that $V(t)$ must be continuous
+ $i(t)$ can be stepwise.

② Analyze $t > 0$


↳ Find $V(0)$, $V(\infty)$, R_{TH} (using tricks)

↳ Plug into formula.

Redraw circuits! Esp. if switches.

RL circuits:

① Discharge of an RL circuit

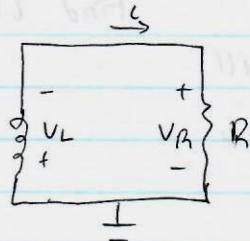


KVL along circuit:

$$V_L + V_R = 0$$

$$L \frac{di}{dt} + \cancel{iR} = 0$$
$$\int_0^t \frac{di}{i} = - \int_0^t \frac{R}{L} dt$$

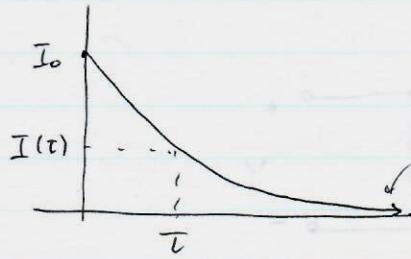
$$\left. \begin{aligned} I(t) &= I_0 e^{-\frac{Rt}{L}} \\ &= I_0 e^{-\frac{t}{\tau}} \\ \tau &= \frac{L}{R} \end{aligned} \right\}$$



All energy stored in inductor is dissipated by resistor

RL circuit problems: find $i(t)$ first. $\Rightarrow \mathcal{T} + I_0$


-Ex://

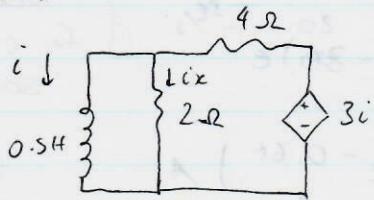

Assume $i(0) = 10A$. Find $i(t)$ and $i_x(t)$

Want to find \mathcal{T} :

Find R_{Th} :

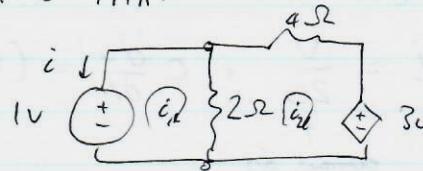

Use KVL:

$$\begin{aligned} \textcircled{1}: \quad 1 - 2(i_1 - i_2) &= 0 \\ \textcircled{2}: \quad -2(i_2 - i_1) + 4(i_2) + 3i_1 &= 0 \end{aligned}$$

$$\left. \begin{aligned} i_1 &= -3A \\ i &= 3A \end{aligned} \right\}$$

Mesh analysis
for R_{Th}
shorts well.

$$\therefore R_{Th} = \frac{V_0}{i_1} = \frac{1}{3} \Omega$$

$$\therefore \mathcal{T} = \frac{L}{R} = \frac{1}{2} \times 3 = \frac{3}{2}$$

$$\therefore i(t) = 10e^{-\frac{2}{3}t}$$


To find i_x :

$$i_x = \frac{3(10e^{-\frac{2}{3}t})}{2} = 15$$

Voltage along inductor $\rightarrow L \cdot \frac{di}{dt} = -\frac{10}{3}e^{-\frac{2}{3}t}$ Find voltage first.


$$i_x = \frac{V}{2} = -\frac{5}{3}e^{-\frac{2}{3}t} A$$

-Ex://

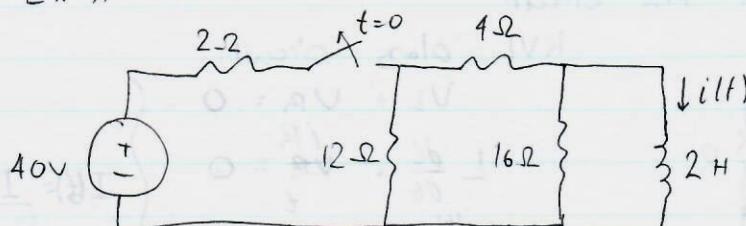

Find $i(t)$ for $t > 0$

$t < 0$:

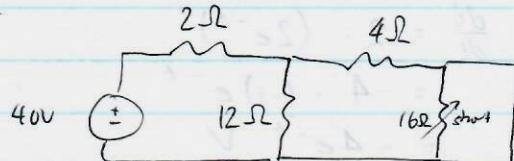

We want to find $i(0) = i(0^-)$
 ↳ Find i of 4Ω .

$$12\Omega \parallel 4\Omega \Rightarrow R_{eq} = 3\Omega$$


$$\therefore I_T = \frac{40}{3} = 8A$$

$$\text{Voltage division: } V_{2\Omega} = 40 \cdot \frac{2}{3} = 16V$$

24 V across 4Ω :

$$\therefore i(0) = \frac{24}{4} = 6A \Rightarrow i(0)!$$


$t > 0$:

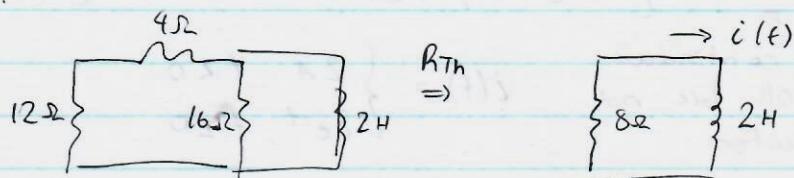

$$\therefore T = \frac{L}{R} = \frac{2}{8} = \frac{1}{4}s$$


$$\therefore i(t) = 6e^{-4t} A$$

- Ex://

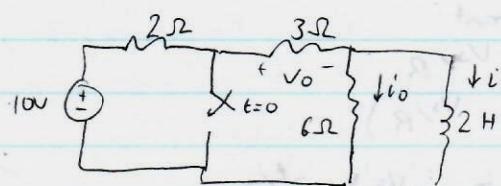

Find i_0, v_0, i for all time.

$t < 0$:

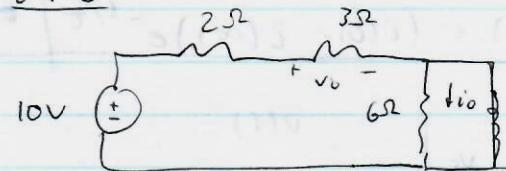


$$v_0 = 10 \cdot \frac{3}{5} = 6V$$

$$i(0) = i(0^-) = \frac{10}{5} = 2A$$

$$i_0 = 0$$

$t > 0$:

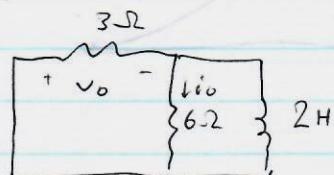

$$3\Omega \parallel 6\Omega \Rightarrow R_{Th} = 2\Omega$$

$$\therefore T = \frac{L}{R} = 1s$$

$$\therefore i(t) = 2e^{-t} A$$

$$i_0 = 2e^{-t} \times \frac{1}{3} = \frac{2}{3}e^{-t}$$

Not proper b/c no ita
 Which direction is in-

Instead, find V from inductor
 + apply to problem.

Trying another option:

$$v_L = L \cdot \frac{di}{dt} = 2 \cdot (2e^{-t})' \\ = 4 \cdot (-1)e^{-t} \\ = -4e^{-t} V$$

$$\therefore v_0 = -v_L = 4e^{-t}$$

$$i_0 = v_L/6 = -2/3 e^{-t}$$

Conclusion:


$$i_0(t) = \begin{cases} 0 & t < 0 \\ -2/3 e^{-t}, & t \geq 0 \end{cases}, \quad v_0(t) = \begin{cases} 6V & t < 0 \\ 4e^{-t} V, & t \geq 0 \end{cases}$$

Not continuous,
but OIC b/c not
inductor

$$i(t) = \begin{cases} 2A, & t < 0 \\ 2e^{-t}, & t \geq 0 \end{cases}$$

Not continuous.

② Charging an RL circuit

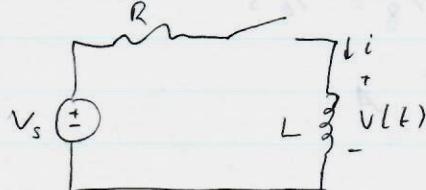

$$i = i_t + i_{ss} \\ = Ae^{-t/\tau} + \frac{V_s}{R}$$

After long time,
inductor = short



Let i_0 = initial current:

$$I_0 = A + \frac{V_s}{R}$$


$$\therefore A = (I_0 - \frac{V_s}{R})$$

$$\therefore i(t) = \frac{V_s}{R} + (I_0 - \frac{V_s}{R}) e^{-t/\tau}$$
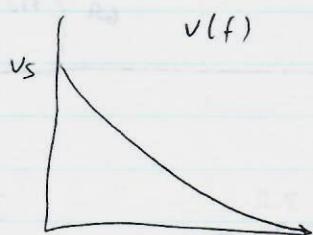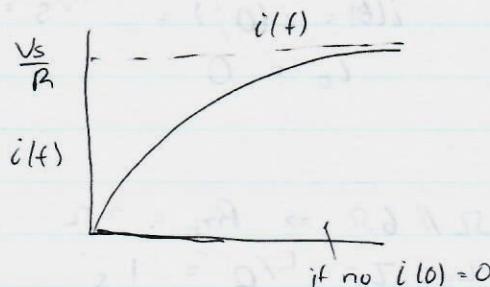
$$i(t) = i(\infty) + (i(0) - i(\infty)) e^{-t/\tau} \quad \leftarrow \text{Same as RC!}$$




- Ex://

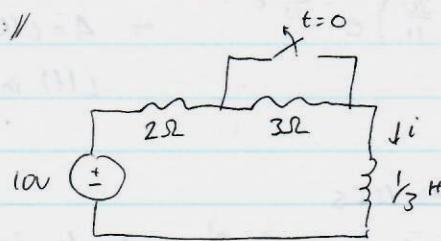


Find $i(t)$ for all time.

$t < 0$:
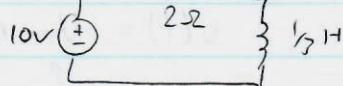
$$\Rightarrow i(0) = i(0^-) = \frac{10}{2} = 5A$$



$t > 0$:

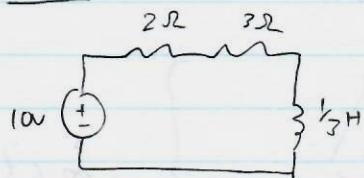


$$i(\infty) = \frac{10}{5} = 2A$$

$$T = \frac{L}{R_{TH}} = \frac{1}{3} \times \frac{1}{5} = \frac{1}{15} s$$

$$\begin{aligned} i(t) &= 2 + (5 - 2) e^{-15t} A \\ &= 2 + 3 e^{-15t} A \end{aligned}$$

- Ex://

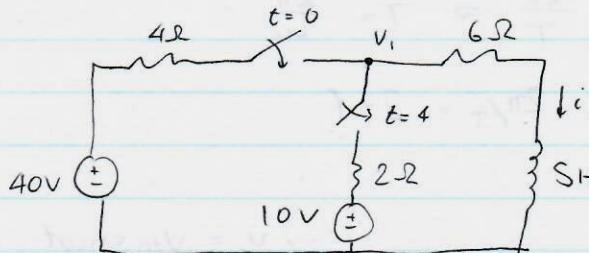


Find $i(t)$ for all time.

$t < 0$:

No closed switches $\Rightarrow i(0) = 0$

$0 < t < 4$:

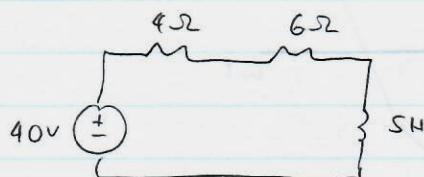

$$i(\infty) = \frac{40}{10} = 4A$$

$$T = \frac{L}{R_{TH}} = 0.5 s$$

$$\begin{aligned} i(t) &= 4 + (-4) e^{-2t} \\ &= 4(1 - e^{-2t}) \end{aligned}$$

$t > 4$:

$$\begin{aligned} R_{TH} &= 4\Omega \parallel 2\Omega + 6\Omega \\ &= 2\frac{2}{3}\Omega \end{aligned} \quad \Rightarrow \quad T = \frac{L}{R_{TH}} = \frac{15}{22} s$$

Find $i(\infty)$:

$$\frac{V_1 - 40}{4} + \frac{V_1 - 10}{2} + \frac{V_1}{6} = 0 \Rightarrow V_1 = \frac{180}{11} V$$

$$\therefore i(\infty) = \frac{V_1}{6} = \frac{30}{11} A$$


Hilary

$$i(t) = \frac{30}{\pi} + \left(4 - \frac{30}{\pi}\right) e^{-\frac{22}{15}t} \Rightarrow 4 = i(0) \text{ from } i(t) \text{ in } t < 4.$$

STEADY-STATE SINUSOIDAL ANALYSIS

Sinusoid:
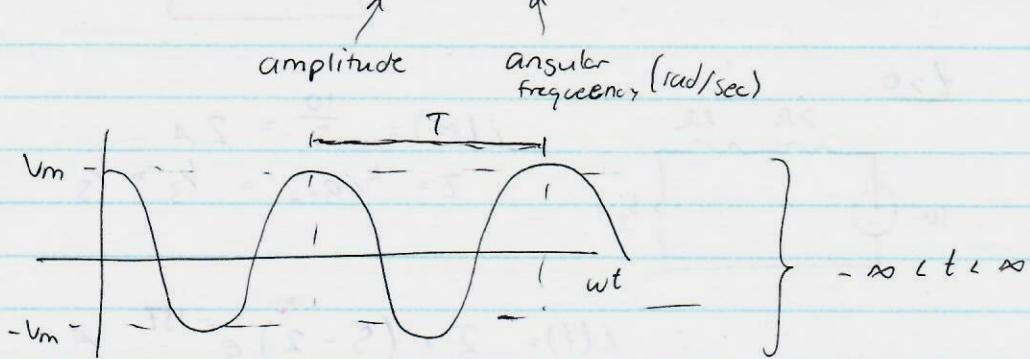
$$v(t) = V_m \cos(\omega t + \theta) \quad \begin{matrix} \text{phase angle in rad.} \\ \text{(shift)} \end{matrix}$$




Period: how many sec. for one rotation?

$$\omega = \frac{2\pi}{T} \Rightarrow T = \frac{2\pi}{\omega}$$

Frequency: $1/T \rightarrow \omega = 2\pi/T = 2\pi f$

Phase:

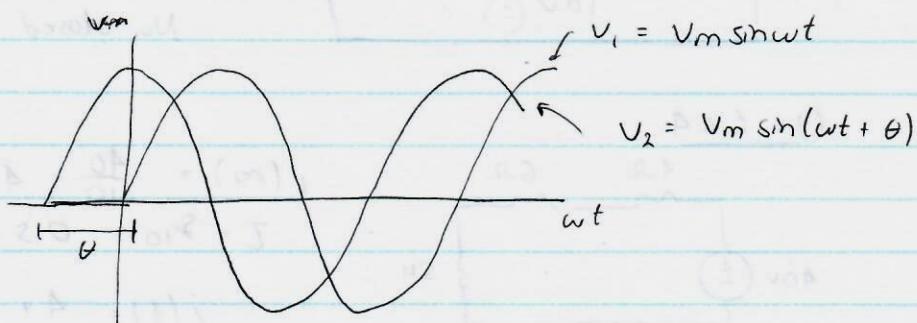


v_2 leads v_1 by θ , and v_1 lags v_2 by θ

In-phase: $\theta = 0 \Rightarrow$ reach max/min at same time.

Convert $\sin \leftrightarrow \cos$ + combine trig functions:

Graphical formula:

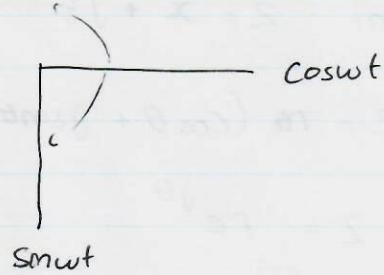


$$\Rightarrow \begin{aligned} \cos(wt \pm 90^\circ) &= \pm \sin(wt) \\ \cos(wt \pm 180^\circ) &= -\cos(wt) \\ \sin(wt \pm 180^\circ) &= -\sin(wt) \\ \sin(wt \pm 90^\circ) &= \cos(wt) \end{aligned}$$

Combine: 117 knowledge:

$$A \cos wt + B \sin wt = C \cos(wt - \theta)$$
$$C = \sqrt{A^2 + B^2} \quad \theta = \tan^{-1}(B/A)$$

Ex:// $3\cos(wt) - 4\sin wt = - \dots \cos$

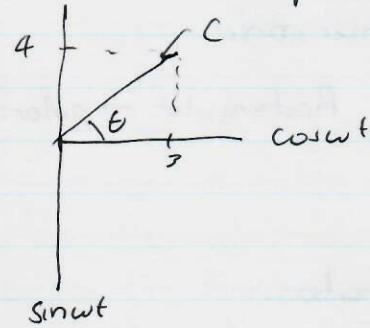①: Draw graphical: make points on graph corresponding to functions.



②: Find C and θ :

$$C = \sqrt{4^2 + 3^2} = 5$$

$$\theta = \tan^{-1}(-4/3) = -53.1^\circ$$

$$\therefore 3\cos wt - 4\sin wt = 5 \cos(wt + 53.1^\circ)$$

PHASORS

Complex # that represents sinusoid:

- Complex # review:

$$j = \sqrt{-1} \Rightarrow j^2 = -1$$

Hilary

Complex numbers: $z = x + jy$


Real

Imaginary

Rectangular form: $z = x + jy$

Polar form: $z = r(\cos\theta + j\sin\theta) = r\angle\theta$

Exponential: $z = re^{j\theta}$

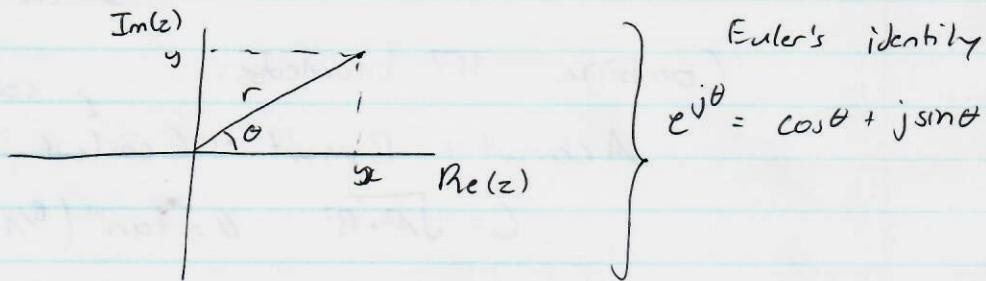

$$\cos\theta = \frac{e^{j\theta} + e^{-j\theta}}{2}, \quad \sin\theta = \frac{e^{j\theta} - e^{-j\theta}}{2j}$$

Conversions:

Rectangular \rightarrow polar: $x = r\cos\theta, \quad y = r\sin\theta$

$$r = \sqrt{x^2 + y^2}, \quad \theta = \tan^{-1}(\frac{y}{x})$$

Operations:

Addition + subtraction: use rectangular coordinates:

$$\begin{aligned} z_1 \pm z_2 &= (x_1 \pm jy_1) + (x_2 \pm jy_2) \\ &= (x_1 \pm x_2) + (y_1 \pm y_2)j \end{aligned}$$

Multiplication / division: use polar:

$$z_1 z_2 = r_1 r_2 \angle(\theta_1 + \theta_2)$$

$$z_1/z_2 = \frac{r_1}{r_2} \angle(\theta_1 - \theta_2)$$

Conjugate: $z^* = x - yj$ (division in rectangular).

$v(t) = V_m \cos(\omega t + \theta)$ \rightarrow Time domain rep.

\hookrightarrow Phasor = $\boxed{V_m e^{j\theta}} = V_m \angle \theta$ \Rightarrow Complex number.

\hookrightarrow Phasor-domain representation

Ex://

Chart for phasors:

Based on $\text{Re}(z)$

$$v(t) = V_m \cos(\omega t + \theta) \Leftrightarrow V_m e^{j\theta} = V_m \angle \theta$$

$$V_m \sin(\omega t + \theta) \Leftrightarrow V_m \angle \theta - 90^\circ$$

$$I_m \cos(\omega t + \theta) \Leftrightarrow I_m \angle \theta$$

$$I_m \sin(\omega t + \theta) \Leftrightarrow I_m \angle \theta - 90^\circ$$

Differentiation / integration:

$$\boxed{\begin{array}{c} \frac{dv}{dt} = j\omega v \\ \text{Time domain} \qquad \qquad \qquad \text{Phasor} \end{array}} \quad (\text{multiply phasor by } j\omega \text{ for dif.})$$

$$\boxed{\begin{array}{c} \int v dt = \frac{v}{j\omega} \\ \text{Time} \qquad \qquad \qquad \text{Phasor} \end{array}}$$

- Ex:// Convert sinusoids to phasors:

a) $i = 6 \cos(50t - 40^\circ)$

$$i_m = 6 \Rightarrow \theta = -40^\circ \Rightarrow \tilde{i} = 6 \angle -40^\circ$$

b) $v = -4 \sin(30t + 50^\circ)$

Real but defined in terms of sh. Real \rightarrow cos!

①: Cos conversion:

$$v = -4 \sin(30t + 50^\circ) = 4 \cos(30t + 140^\circ)$$

$$\therefore \tilde{v} = 4 \angle 140^\circ$$

- Ex:// Find sinusoids described by phasors:

a) $\tilde{I} = -3 + 4j \text{ A}$

Converting to polar:

$$-3 + 4j = 5 (\cos 126.87^\circ + j \sin 126.87^\circ)$$

$$\therefore \tilde{I} = 5 \angle 126.87^\circ$$

- Sinusoid:

$$I = 5 \cos(\omega t + 126.87^\circ) \text{ A}$$

b) $\tilde{V} = j8e^{-j20^\circ} \text{ V}$

2 complex # multiplied together!

1. $j \Rightarrow 1 \angle 90^\circ$

2. $8e^{-j20^\circ} \Rightarrow 8 \angle -20^\circ$

∴ Multiply:

$$j8e^{-j20^\circ} = (1 \angle 90^\circ)(8 \angle -20^\circ)$$

$$= 8 \angle 90 - 20^\circ$$

$$= 8 \angle 70^\circ$$

$$\therefore V(t) = 8 \cos(\omega t + 70^\circ) \text{ V}$$

We cannot find ω from phasor.

- Adding currents / voltage waveforms is easy using phasors

1. Convert to phasor

2. Convert to rectangular form + add

3. Convert back to sinusoid.

phasors.

- Integro-differential equations: remember integration \rightarrow differentiation for

o Ex:// Determine $i(t)$ if:

$$4i + 8 \int i dt - 3 \frac{di}{dt} = 50 \cos(2t + 75^\circ)$$

We know from RHS that $\omega = 2$

$$\therefore 4\tilde{I} + 8 \cdot \frac{\tilde{I}}{2j} - 3\tilde{I} \cdot 2j = 50 \angle 75^\circ$$

$$\tilde{I} (4 + 4j - 6j) = 50 \angle 75^\circ$$

Let's solve \tilde{I} using complex # division.

PHASORS + CIRCUIT ELEMENTS

Resistor: Ohm's Law holds:

$$\boxed{\tilde{V} = R \tilde{I}}$$

Inductor:

In a normal circuit: $V = L \cdot \frac{di}{dt}$

In an AC circuit:

$$\boxed{\tilde{V} = L \cdot j\omega \tilde{I}} \Rightarrow \begin{matrix} \text{Phase of } \tilde{V} \text{ is } 90^\circ \text{ out} \\ \text{of phase w/ } \tilde{I} \text{ (current} \\ \text{lags by } 90^\circ \text{)} \end{matrix}$$

Capacitor:

In a normal circuit: $i = C \cdot \frac{dv}{dt}$

In an AC circuit:

$$\boxed{\tilde{I} = C \cdot j\omega \tilde{V}} \Rightarrow \begin{matrix} \text{Phase of } \tilde{I} \text{ is } 90^\circ + \phi \\ \text{or (current leads by } 90^\circ \text{)} \end{matrix}$$

- Ex:// $V = 12 \cos(60t + 45^\circ)$ \rightarrow 0.1-H inductor. Find current.

①. Convert to phasor:

$$\tilde{V} = 12 \angle 45^\circ$$

②: Use the inductor formula:

$$\tilde{V} = L \cdot j\omega \tilde{I}$$

$$\tilde{I} = \frac{12 \angle 45^\circ}{j\omega L} = \frac{12 \angle 45^\circ}{j \cdot 60 \cdot 0.1} = \frac{12 \angle 45^\circ}{6 \angle 90^\circ}$$

Conversion!

$$= 2 \angle -45^\circ$$

$$\therefore \tilde{I}(t) = 2 \cos(60t - 45^\circ)$$

IMPEDANCE + ADMITTANCE

$$\tilde{U} = R \tilde{I} \quad U = j\omega L \tilde{I} \quad \tilde{V} = \frac{\tilde{I}}{j\omega C}$$

$$\Downarrow \quad \Downarrow \quad \Downarrow$$

$$\frac{\tilde{U}}{\tilde{I}} = R \quad \frac{\tilde{U}}{\tilde{I}} = j\omega L \quad \frac{\tilde{V}}{\tilde{I}} = \frac{1}{j\omega C}$$

Impedance: $Z = \frac{\tilde{U}}{\tilde{I}} = \frac{\tilde{V}}{\tilde{I}} \Rightarrow$ Opposition to flow of sinusoidal current.

Impact of frequency on impedance.

$\omega \rightarrow 0$ (DC circuit):

$$Z_L \rightarrow 0, \quad Z_C \rightarrow \infty \quad (L: \text{short circuit}, C: \text{open circuit})$$

$\omega \rightarrow \infty$:

$$Z_L \rightarrow \infty, \quad Z_C \rightarrow 0 \quad (L: \text{open circuit}, C: \text{short circuit})$$

Alternative rep. of impedance:

B/C impedance is a complex \star :

$$Z = R \pm jX$$

$$R = \text{Re}(z) = \text{resistance}$$

$$X = \text{Im}(z) = \text{reactance.}$$

$\hookrightarrow X > 0$: inductor, \tilde{I} lags \tilde{U}

$X < 0$: cap., \tilde{I} leads \tilde{U}

All measured in ohms.

$$Z = |z| \angle \theta$$

$$|z| = \sqrt{R^2 + X^2}, \quad \theta = \tan^{-1} \left(\frac{X}{R} \right) \quad \boxed{\text{Remember polar graph}}$$

Admittance:

$$Y = \frac{1}{Z} = \frac{\tilde{I}}{\tilde{V}}$$

$$= G + jB$$

Conductance:

$$G = \frac{R}{R^2 + X^2}$$

$$\text{Susceptance: } B = -\frac{X}{R^2 + X^2}$$

PHASOR KCL + KVL

KCL: At a particular node


$$\sum_n \tilde{I}_n = 0$$

KVL: In a loop:

$$\sum_n \tilde{V}_n = 0$$

} No change!


SERIES + PARALLEL IMPEDANCES

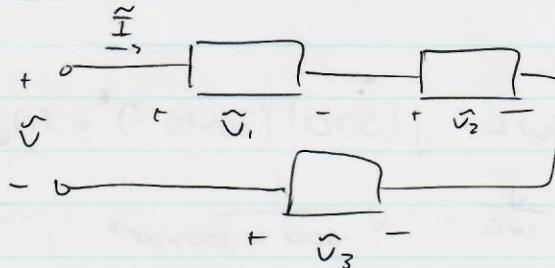

$$\tilde{V} = Z_1 \tilde{I} + Z_2 \tilde{I} + Z_3 \tilde{I}$$

$$\frac{\tilde{V}}{\tilde{I}} = Z_1 + Z_2 + Z_3$$

$$Z_T = Z_1 + Z_2 + Z_3$$

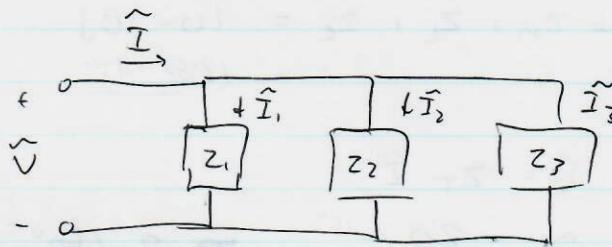

$$\tilde{I} = \tilde{I}_1 + \tilde{I}_2 + \tilde{I}_3$$

$$\frac{\tilde{V}}{Z_T} = \frac{\tilde{V}}{Z_1} + \frac{\tilde{V}}{Z_2} + \frac{\tilde{V}}{Z_3}$$

$$\therefore \frac{1}{Z_T} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}$$

Act exactly like resistors.

All techniques that we learned: nodal, mesh... all apply

CIRCUIT ANALYSIS VIA PHASORS + IMPEDANCE

①: Convert circuit from time-domain \rightarrow phasor.

o All $I, V \rightarrow \tilde{I}, \tilde{V}$


o All elements should have impedances.

②: Solve circuit in phasor domain

③: Convert into time domain

Hilary

- Ex://

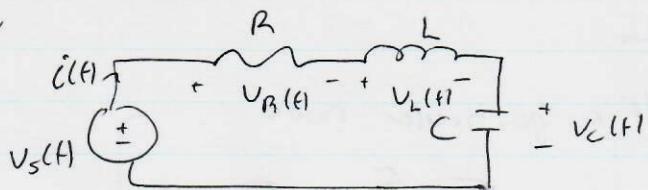

$$R = 10 \Omega$$

$$L = 20 \text{ mH}$$

$$C = 100 \mu\text{F}$$

$$V_s(t) = 20 \cos(500t + 15^\circ)$$

①: Find $i(t)$, $V_R(t)$, $V_L(t)$, $V_C(t)$:

1) Convert $V_s(t)$ to phasor:

$$V_s(t) = 20 \angle 15^\circ$$

2) Find impedances:

$$Z_R = 10$$

$$\text{so } \rightarrow Z_L = j\omega L = j(500)(20 \times 10^{-3}) = 10j$$

$$\text{so } \rightarrow Z_C = -\frac{j}{\omega C} = -j \frac{1}{500 \times 100 \times 10^{-6}} = -20j$$

$$\therefore Z_T = Z_R + Z_L + Z_C = 10 - 10j = 10 \angle -45^\circ$$

3) $i(t)$:

$$\tilde{V} = Z_T \tilde{I}$$

$$\tilde{I} = \frac{20 \angle 15^\circ}{10 \angle -45^\circ} = \text{Hence } 2\sqrt{2} \angle 60^\circ$$

$$= \sqrt{2} \cos(500t + 60^\circ) \text{ A}$$

4) $V_R(t)$:

$$\tilde{V}_R = Z_R \cdot \tilde{I}$$

$$= 10 \cdot \sqrt{2} \angle 60^\circ = 10\sqrt{2} \cos(500t + 60^\circ)$$

5) $V_L(t)$:

$$\tilde{V}_L = Z_L \cdot \tilde{I}$$

$$= 10 \angle 90^\circ \cdot \sqrt{2} \angle 60^\circ$$

$$= 10\sqrt{2} \cos(500t + 150^\circ)$$

6) $V_C(t)$:

$$\tilde{V}_C = Z_C \cdot \tilde{I}$$

$$= 20 \angle -90^\circ \cdot \sqrt{2} \angle 60^\circ$$

$$= 20\sqrt{2} \cos(500t - 30^\circ)$$

- Series resonance:


$$Z_{\text{eq}} = R + Z_L + Z_C = R$$

$$\therefore Z_L + Z_C = 0$$

$$\boxed{\omega L = \frac{1}{\omega C}}$$

This leads to $\tilde{V}_L + \tilde{V}_C = 0$

- Ex://

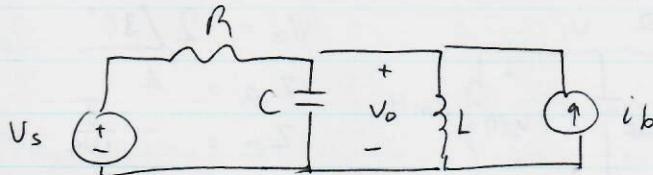

$$V_s = 2 \cos(1000t + 30^\circ)$$

$$i_b = \cos(1000t - 45^\circ)$$

$$R = 4 \Omega, C = 250 \mu\text{F}, L = 2 \text{mH}$$

Find $V_o(t)$:

Perform nodal analysis!

$$\textcircled{1}: V_s \Rightarrow 2 \angle 30^\circ, i_b = 1 \angle -45^\circ$$

$$Z_R = 4, Z_C = -\frac{1}{\omega C} = -4j, Z_L = j\omega L = 2j$$

\textcircled{2}: Nodal:

$$\frac{\tilde{V}_o - \tilde{V}_s}{Z_R} + \frac{\tilde{V}_o}{Z_C} + \frac{\tilde{V}_o}{Z_L} - \tilde{i}_b = 0$$


$$\frac{\tilde{V}_o - \tilde{V}_s}{4} + \frac{\tilde{V}_o}{(-4j)} + \frac{\tilde{V}_o}{2j} - \tilde{i}_b = 0$$

$$j(\tilde{V}_o - \tilde{V}_s) + \tilde{V}_o + 2\tilde{V}_o - 4j\tilde{i}_b = 0$$

$$\left. \begin{aligned} (1+j)V_o &= j\tilde{V}_s + 4j\tilde{i}_b \\ &= (1 \angle 90^\circ)(2 \angle 30^\circ) + (4 \angle 90^\circ)(1 \angle -45^\circ) \\ &= 2 \angle 120^\circ + 4 \angle 45^\circ \end{aligned} \right\} \text{Only plus in } V + I \text{ phasor @ end-}$$

$$V_o = \frac{2 \angle 120^\circ + 4 \angle 45^\circ}{\sqrt{2} \angle 45^\circ}$$

- Ex://

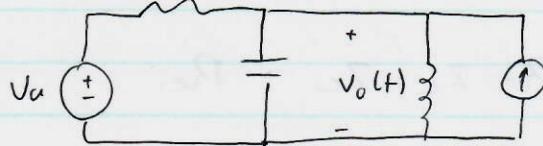

$$V_a = 2 \cos(1000t + 30^\circ)$$


$$i_b = \cos(2000t - 45^\circ)$$

$$R = 4 \Omega, C = 250 \mu F, L = 2 mH$$

Find $V_o(t)$

Since there are different angular frequencies \Rightarrow superposition.

①: Just for V_a :

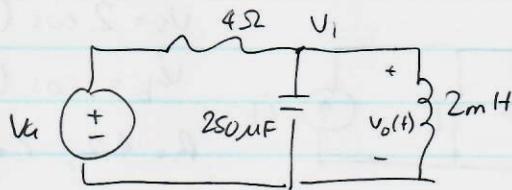

$$V_a = 2 \angle 30^\circ$$

$$Z_R = 4$$

$$Z_C = -\frac{1}{\omega C} = -4j$$

$$Z_L = j\omega L = 2j$$

$$\therefore \frac{\tilde{V}_1 - \tilde{V}_a}{4} + \frac{\tilde{V}_1}{Z_C} + \frac{\tilde{V}_1}{Z_L} = 0$$


$$\frac{\tilde{V}_1 - 2 \angle 30^\circ}{4} + \frac{\tilde{V}_1 j}{4} - \frac{\tilde{V}_1 j}{2} = 0$$

$$\tilde{V}_1 - 2 \angle 30^\circ + \tilde{V}_1 j - 2 \tilde{V}_1 j = 0$$

$$\tilde{V}_1 (1 - j) = 2 \angle 30^\circ$$

$$\tilde{V}_1 = \frac{2 \angle 30^\circ}{\sqrt{2} \angle 45^\circ} = \frac{2}{\sqrt{2}} \angle 75^\circ = \sqrt{2} \angle 75^\circ$$

②: Just for i_b :

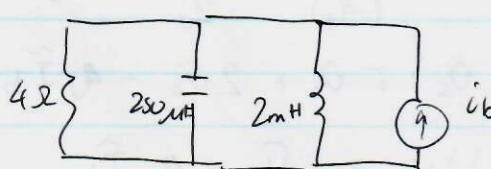

$$i_b = 1 \angle -45^\circ$$

$$\frac{\tilde{V}_2}{4} + \frac{\tilde{V}_2 j}{4} - \frac{\tilde{V}_2 j}{2} - \frac{1 \angle 45^\circ}{2} = 0$$

$$\tilde{V}_2 = \frac{4}{\sqrt{2}} \cos(2000t - 90^\circ)$$

$$\therefore V_o(t) = \tilde{V}_1 + \tilde{V}_2 = \sqrt{2} \cos(1000t + 75^\circ)$$


$$+ \frac{4}{\sqrt{2}} \cos(2000t - 90^\circ)$$

- Resonance:

$$Z = j\omega L \parallel \frac{1}{j\omega C} \Rightarrow \text{Can be used as a resonance circuit.}$$

$$= \frac{j\omega L \cdot \frac{1}{j\omega C}}{j\omega L - j\frac{1}{\omega C}} = \frac{\frac{L}{C}}{j(\omega L - \frac{1}{\omega C})}$$

$$\therefore |Z| = \frac{\frac{L}{C}}{|\omega L - \frac{1}{\omega C}|} \Rightarrow$$

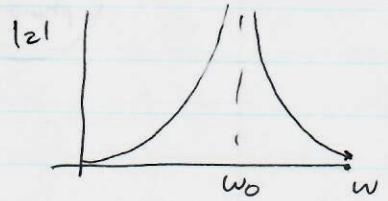


$$\omega \rightarrow 0 \Rightarrow |Z| \rightarrow 0, \quad \omega \rightarrow \infty \Rightarrow |Z| \rightarrow 0$$

$$\text{If } |Z| \rightarrow \infty \text{ iff } |\omega L - \frac{1}{\omega C}| \rightarrow 0$$

$$\text{Recall: } \omega_0 L = \frac{1}{\omega_0 C}$$

$$\boxed{\omega_0 = \pm \frac{1}{\sqrt{LC}}} \rightarrow \text{Resonance frequency}$$

At ω_0 :

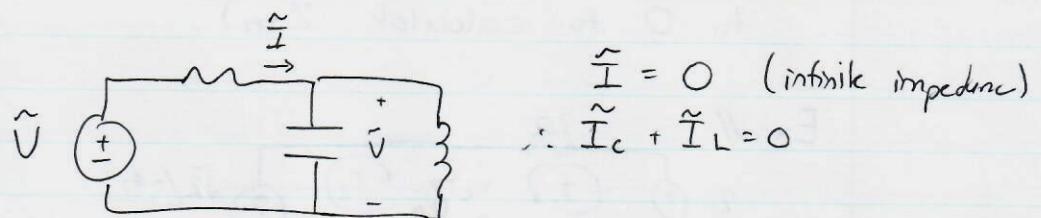


$$\tilde{I} = 0 \text{ (infinite impedance)} \\ \therefore \tilde{I}_C + \tilde{I}_L = 0$$

Recall: $C + L$ have the same voltage \tilde{V} :


$$\begin{aligned} \tilde{I}_C &= \frac{\tilde{V}}{R_C} = \frac{\tilde{V}}{j\omega C} = j\sqrt{\frac{C}{L}} \\ \tilde{I}_L &= \frac{\tilde{V}}{Z_L} = \frac{\tilde{V}}{j\omega L} = -j\sqrt{\frac{C}{L}} \end{aligned} \quad \left. \right\} \tilde{V}_0 = \tilde{V} \text{ (max.)}$$

- Source transformation

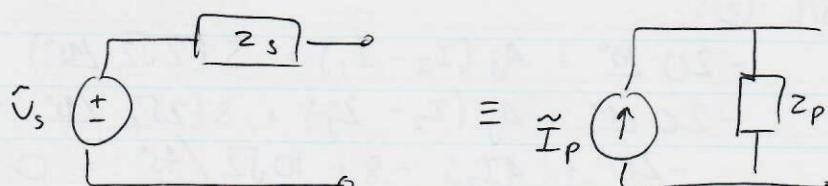


$$\begin{aligned} ① \quad Z_p &= Z_s \\ ②: \quad \tilde{V}_s &= Z_p \tilde{I}_p \end{aligned} \quad \left. \right\} \text{Exactly like DC source transform.}$$

THEVENIN + NORTON IN PHASOR DOMAIN

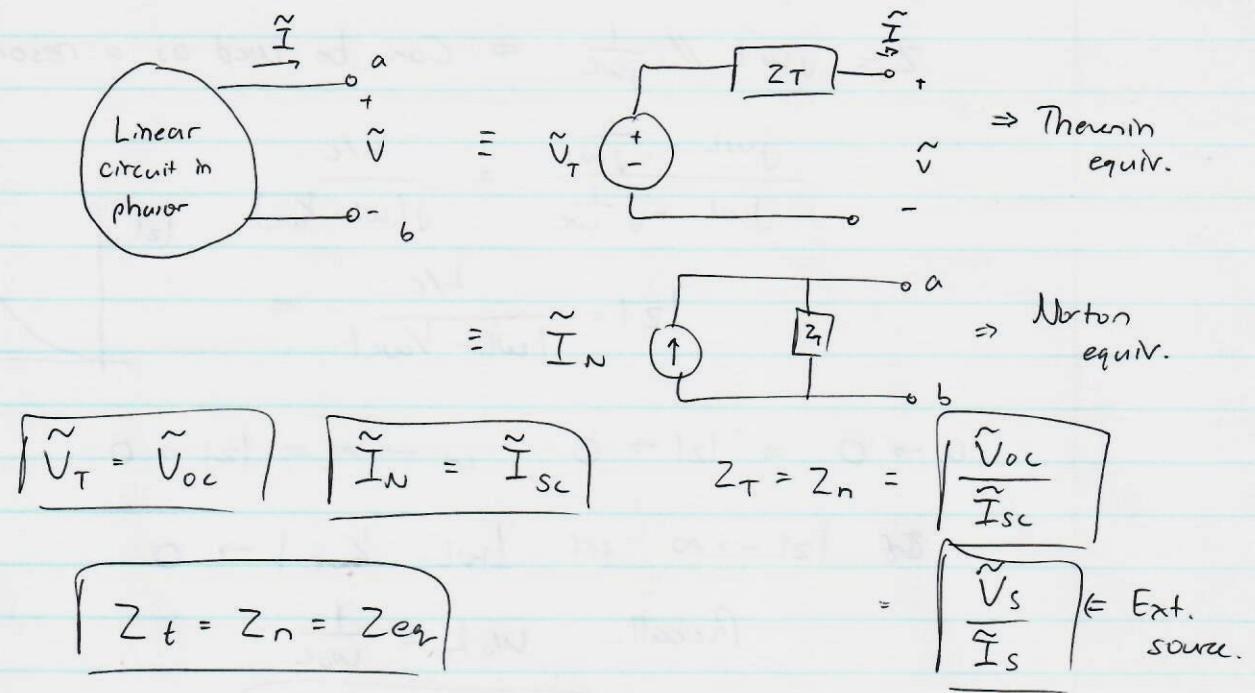

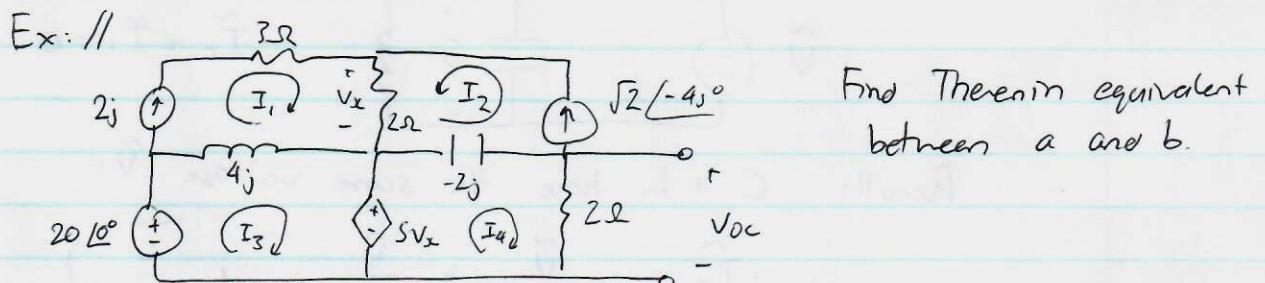Some tips in DC apply in AC (e.g. set indep. sources to 0 to calculate Z_{th})



$$I_1 = 2j, \quad I_2 = \sqrt{2} \angle -45^\circ \Rightarrow V_x = 2(I_1 + I_2)$$

$$= 2(2j + 1-j)$$

$$= 2 - 2j$$

$$= 2\sqrt{2} \angle 45^\circ$$

KVL (3):

$$-20 \angle 10^\circ + 4j(I_3 - I_1) + 5(2\sqrt{2} \angle 45^\circ) = 0$$

$$-20 \angle 10^\circ + 4j(I_2 - 2j) + 5(2\sqrt{2} \angle 45^\circ) = 0$$

$$-20 + 4I_3j + 8 + 10\sqrt{2} \angle 45^\circ = 0$$

$$I_3 = \frac{2 - 10j}{4j} = 2.55 \angle -168.7^\circ$$

KVL ④:

$$-5V_x - 2j(I_4 - I_2) + 2I_4 = 0$$

$$\therefore I_4 = 6j$$

$$V_{OC} = V_x = 2I_4 = \boxed{12j}$$

Finding \tilde{I}_{SC} \Rightarrow Changes KVL 4 \Rightarrow short circuiting 2Ω resistor.

$$-5V_x - 2j(I_4 - I_2) = 0$$

$$I_4 = \frac{12}{\sqrt{2}} \angle 135^\circ = I_{SC}$$


$$Z_T = \frac{\tilde{V}_{OC}}{\tilde{I}_{SC}} = \frac{12 \angle 90^\circ}{\frac{12}{\sqrt{2}} \angle 135^\circ} = \sqrt{2} \angle -45^\circ = \boxed{1-j}$$

OP-AMPS IN PHASOR DOMAIN

Pretty much same analysis as DC Op Amp

1. Look at $\tilde{V}_p + \tilde{V}_n \Rightarrow$ possible relation to \tilde{V}_o
2. Construct nodal equations
3. Look for common op-amp (inverting, non-inverting, adding, difference, voltage follower)

Ex://

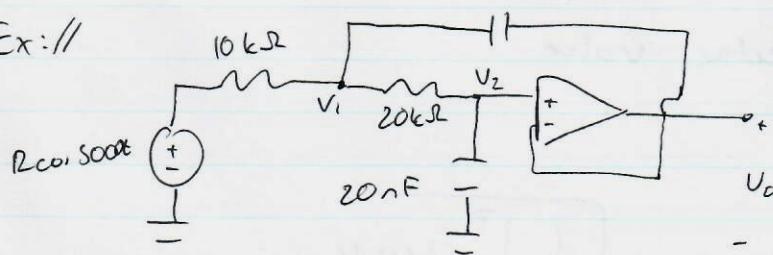

Find V_o :

①: Convert to phasor domain:

$$V_s = 12\cos(5000t) = 12 \angle 0^\circ$$

$$C_1 = 10nF \Rightarrow -20j, C_2 = 20nF \Rightarrow -10j$$

⑦: Find relations:

$$V_n = V_0 \Rightarrow V_p = V_2 = V_0$$

⑧: Nodal:

$$1) \frac{V_1 - V_s}{10} + \frac{V_1 - V_0}{-20j} + \frac{V_1 - V_0}{20}$$

$$2) \frac{V_0 - V_1}{10} + \frac{V_0}{-10j} = 0$$

$$\therefore V_0 = 4 \angle -90^\circ = 4 \sin(5000t)$$

Root-Mean-Squared Value (RMS):

$$\begin{array}{c} \overbrace{V(t)}^0 \\ \overbrace{0}^0 \end{array} \quad \left\{ R \right\} \Rightarrow P_{\text{absorbed}} = \frac{V^2(t)}{R}$$
$$P_{\text{avg}} = \frac{1}{T} \int_0^T \frac{V^2(t)}{R} dt \Rightarrow 117!$$

$$P_{\text{avg}} = \frac{1}{R} \left(\sqrt{\frac{1}{T} \int_0^T V^2(t) dt} \right)^2$$
$$\quad \quad \quad \underbrace{\sqrt{\frac{1}{T} \int_0^T V^2(t) dt}}_{V_{\text{RMS}}}$$

$$\therefore \boxed{P_{\text{avg}} = \frac{V_{\text{RMS}}^2}{R}} \Rightarrow \boxed{V_{\text{RMS}} = \sqrt{\frac{1}{T} \int_0^T V^2(t) dt}}$$

RMS \Rightarrow effective value

Similarly:

$$I_{\text{RMS}} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$
$$\therefore \boxed{P_{\text{avg}} = R \cdot I_{\text{RMS}}^2}$$


RMS For SINUSOIDS

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

For a function that is non-sinusoidal but periodic:
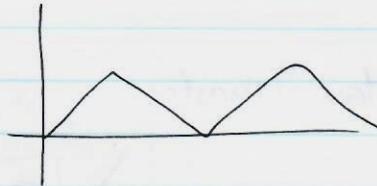
$$V_{rms} = \frac{V_m}{\sqrt{3}}, \quad I_{rms} = \frac{I_m}{\sqrt{3}} \Rightarrow \text{Triangular!}$$



→ Triangular function.

How do you find RMS for sums of functions?

$$\text{Ex: } v(t) = V_m_1 \cos(\omega_1 t + \theta_1) + V_m_2 \cos(\omega_2 t + \theta_2)$$

1) If $\omega_1 \neq \omega_2$


$$\therefore V_{rms} = \sqrt{V_{rms_1}^2 + V_{rms_2}^2}$$

2) If $\omega_1 = \omega_2$

$$V_{rms} = \sqrt{V_{rms_1}^2 + V_{rms_2}^2 + V_m_1 V_m_2 \cos(\theta_1 - \theta_2)}$$

If DC $\Rightarrow V_{rms} = V_{DC}$ (no $\div \sqrt{2}$)

MAX POWER TRANSFER

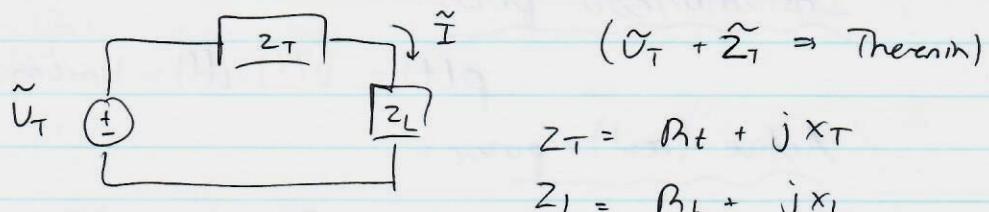

$$(V_T + Z_T \Rightarrow \text{Thermal})$$

Max avg power transfer happens when:

$$R_L = R_T \quad \wedge \quad X_L = -X_T$$

Hilary

$\hookrightarrow Z_T$ is inductive $\Rightarrow Z_L$ is capacitive

Z_T is capacitive $\Rightarrow Z_L$ is inductive

$$P_{\max} \text{ of } L: \quad P_{\max} = \frac{|\tilde{V}_t|^2}{8R_t}$$

If $Z_L = R_L$ (real circuit element)

$$\Rightarrow R_L = |Z_t| = \sqrt{R_t^2 + X_t^2} +$$

$$\Rightarrow P_{\max} = \frac{1}{2} |\tilde{I}|^2 R_L = I_{\text{rms}}^2 \cdot R_L$$

Max Transfer

$$Z_L \in \mathbb{C}$$

$$Z_L \in \mathbb{R}$$


$$Z_L = R_t - X_t j$$

$$R_L = \sqrt{R_t^2 + X_t^2}$$

$$P_{\max} = \frac{(\tilde{V}_t)^2}{8R_t}$$

$$P_{\max} = I_{\text{rms}}^2 \cdot R_L$$

Different Power Types

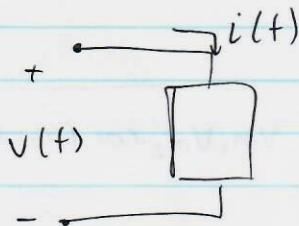

$$v(t) = V_m \cos(\omega t + \theta_v)$$

$$i(t) = I_m \cos(\omega t + \theta_i)$$

Subtract θ_i from both equations

$$v(t) = V_m \cos(\omega t + \theta_v - \theta_i)$$

$$i(t) = I_m \cos(\omega t + \theta_i)$$

Instantaneous power:

$$p(t) = v(t) \cdot i(t) = V_m I_m \cos(\omega t + \theta_v - \theta_i) \cos(\omega t)$$

Active (real) power:

$$P = V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_i) \text{ (watts)}$$

↳ electric energy \rightarrow non-electric energy

Reactive power

$$Q = V_{rms} I_{rms} \sin(\theta_v - \theta_i) \quad \begin{matrix} \text{volts} \\ \text{amps} \\ \text{or reactive.} \end{matrix} \quad (V-A-R)$$

↳ Not transformed to non-electric energy, transferred between elements.

Linking equations:

$$P(t) = P + P \cos(2\omega t) - Q \sin(2\omega t)$$

Also $P_{avg} = P$ (active power)

Power factor: $\rho_f = \cos(\theta_v - \theta_i)$

$$\begin{aligned} P &= V_{rms} I_{rms} \cdot \rho_f & \begin{matrix} \text{V as} \\ \text{leads} \end{matrix} \tilde{I} \text{ lags } \tilde{V} / Q > 0 \\ &= I_2 V_m I_m (\rho_f) & \begin{matrix} \text{leads} \\ \text{I leads } \tilde{V} / Q < 0 \end{matrix} \end{aligned}$$

POWER IN A RESISTOR

$\theta_v \leftrightarrow \theta_i \Rightarrow$ equal to each other.

$$\therefore \rho_f = \cos(\theta_v - \theta_i) = \cos(0) = 1$$

$$P = \frac{1}{2} V_m I_m = \frac{1}{2} \frac{V_m^2}{R} = \frac{1}{2} I_m^2 R$$

All normal formulas work.

$$Q = V_{rms} I_{rms} \sin(\theta_v - \theta_i) = 0$$

POWER IN AN INDUCTOR

$$\theta_v - \theta_i = 90^\circ \Rightarrow \rho_f = \cos(90^\circ) = 0$$

$$\therefore P = 0$$

$$Q = \frac{1}{2} V_m I_m = \frac{1}{2} (\omega L I_m) I_m = \frac{1}{2} \omega L I_m^2 = \boxed{\frac{\omega L I_{rms}^2}{2}}$$

$$\text{OR } Q = \frac{1}{2} \left(\frac{I_m}{\omega L} \right) V_m = \frac{1}{2} \frac{V_m^2}{\omega L} = \boxed{\frac{V_{rms}^2}{\omega L}}$$

No energy stored \Rightarrow stored in one half of cycle + then release.

POWER IN A CAPACITOR

$$\theta_v - \theta_i = -90^\circ \Rightarrow \begin{aligned} \cos(\theta_v - \theta_i) &= 0 \\ \sin(\theta_v - \theta_i) &= -1 \end{aligned}$$

$$\therefore P = 0$$

$$Q = -\frac{1}{2} V_m I_m = -V_{rms} I_{rms} \quad (\text{always negative!})$$

Expanding:

$$\text{In a capacitor: } I = wC V_m$$


$$\therefore Q = -\frac{1}{2} \frac{I_m^2}{wC} = -\frac{I_{rms}^2}{wC}$$

$$\Rightarrow Q = -\frac{1}{2} V_m (wC V_m) = -\frac{1}{2} wC V_m^2 \\ = -wC V_{rms}^2$$

No P absorbed \Rightarrow stored + released in 1 cycle.

COMPLEX POWER
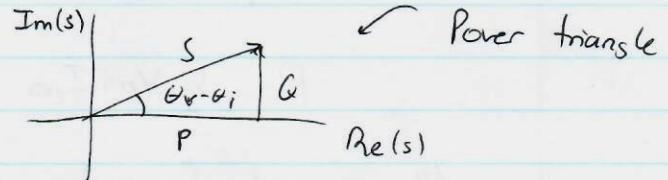
$$S = P + jQ \quad \Rightarrow \quad \begin{matrix} \hookrightarrow [VA] \end{matrix}$$



Notice:

$$\frac{Q}{P} = \frac{\sin(\theta_v - \theta_i)}{\cos(\theta_v - \theta_i)} = \tan(\theta_v - \theta_i)$$

$$\therefore \boxed{\theta_v - \theta_i = \tan^{-1}(\frac{Q}{P}) = \cos^{-1}(pf)}$$

$$\boxed{P_{app} = |S| = \sqrt{P^2 + Q^2} \quad \Rightarrow \quad [VA]}$$


Conjugate of \tilde{I} !:
 $\tilde{I}^* = I_{rms} / \angle \theta_i$

$$S = \frac{1}{2} \tilde{V} \tilde{I}^* = \tilde{V}_{rms} \cdot \tilde{I}_{rms} \Rightarrow |S| = V_{rms} \cdot I_{rms}$$

Remember: $\tilde{V}_{rms} = V_{rms} \angle \theta_v \Rightarrow \tilde{V}_{rms} = \frac{\tilde{V}}{\sqrt{2}}$

$$\tilde{I}_{rms} = I_{rms} \angle \theta_i \Rightarrow \tilde{I}_{rms} = \frac{I}{\sqrt{2}}$$

- Complex power in impedance:

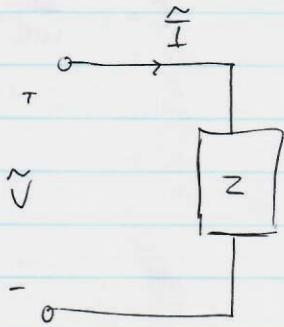

$$\left. \begin{array}{l} \tilde{V} = V_m \angle \theta_v \\ \tilde{I} = I_{rms} \angle \theta_i \\ \tilde{V} = Z \cdot \tilde{I} \end{array} \right\}$$


$$\begin{aligned} S &= \frac{1}{2} \tilde{V} \cdot \tilde{I}^* \\ &= \frac{1}{2} Z \tilde{I} \cdot \tilde{I}^* \\ &= \frac{1}{2} Z \cdot I_{rms} \angle \theta_i \cdot I_{rms} \angle \theta_i \\ &= \frac{1}{2} I_{rms}^2 \cdot Z \\ &= I_{rms}^2 Z \Rightarrow Z = R + jX \\ &= \underbrace{R I_{rms}^2}_P + \underbrace{jX I_{rms}^2}_Q \end{aligned}$$

$$\therefore P = R I_{rms}^2$$


$$Q = X I_{rms}^2 \Rightarrow + \text{ if inductive } Z$$

$$- \frac{1}{\omega C} I_{rms}^2 \Rightarrow - \text{ if capacitive } Z$$

Inductive Z :

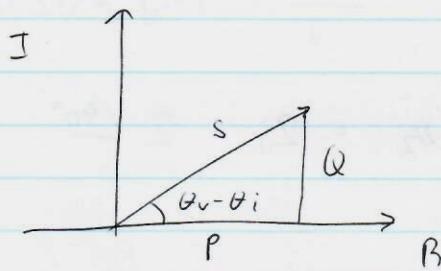


Capacitive Z

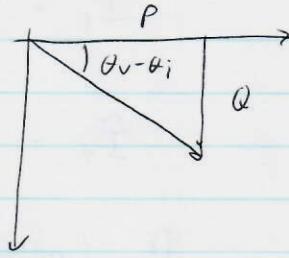

$$\therefore |S| = \sqrt{P^2 + Q^2}$$

$$\tan(\theta_v - \theta_i) = \frac{Q}{P} = \frac{X}{R}$$

- Ex: //

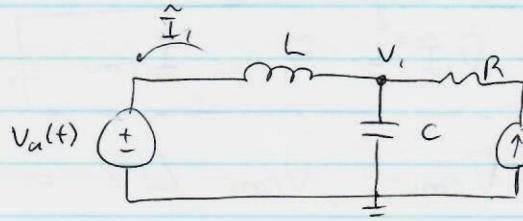

$$V_a(t) = \cos(100t - 90^\circ)$$

$$i_b(t) = \sqrt{2} \cos(100t + 45^\circ)$$

$$R = 1 \Omega \quad L = 100 \text{ H} \quad C = 1 \text{ F}$$

Looking at power of each element:

①: Convert to phasor domain:

$$V_a(t) = 1 \angle -90^\circ = -j \quad R = 1 \Omega \quad C = -\frac{1}{\omega C} j = -j\frac{1}{2}$$

$$i_b(t) = \sqrt{2} \angle 45^\circ = 1+j \quad L = j$$

②: Using nodal analysis to find \tilde{V}_1

$$\frac{\tilde{V}_1 - \tilde{V}_a}{Z_L} + \frac{\tilde{V}_1}{Z_C} = \tilde{I}_b$$

$$\frac{\tilde{V}_1 + j}{j} + \frac{\tilde{V}_1}{-j\frac{1}{2}} = \tilde{I}_b$$

$$-j\tilde{V}_1 + 1 + 2j\tilde{V}_1 = 1+j$$

$$\therefore \tilde{V}_1 = 1 \Rightarrow 1 \angle 0^\circ$$

③: Compute current in each branch + voltage

$$\tilde{I}_1 = \frac{\tilde{V}_1 - \tilde{V}_a}{j} = \frac{1+j}{j} = 1-j = \sqrt{2} \angle -45^\circ$$

$$\tilde{I}_2 = \frac{\tilde{V}_1}{-j\frac{1}{2}} = \frac{1}{-j\frac{1}{2}} = 2j = 2 \angle 90^\circ$$

\tilde{V}_2 (voltage across R):

$$\frac{\tilde{V}_2 - \tilde{V}_1}{R} = \tilde{I}_b(t)$$

$$\tilde{V}_2 - 1 = 1+j$$

$$\tilde{V}_2 = 2+j = \sqrt{5} \angle 26.57^\circ$$

④: Computing power:

1. $\hat{V}_a(t)$:

$$\begin{aligned}
 P_a &= V_{rms} \cdot I_{rms} \cos(\theta_v - \theta_i) \\
 &= \left(\frac{1}{\sqrt{2}}\right) \left(\frac{\sqrt{2}}{\sqrt{2}}\right) \cos(-90^\circ - (-45^\circ)) \\
 &= \frac{1}{\sqrt{2}} \cos(-45^\circ) \\
 &= \frac{1}{\sqrt{2}} \cdot \frac{1}{\sqrt{2}} \\
 &= \boxed{\frac{1}{2} W}
 \end{aligned}$$

$$Q_a = V_{rms} \cdot I_{rms} \cdot \sin(\theta_v - \theta_i)$$

$$\begin{aligned}
 &= \frac{1}{\sqrt{2}} \sin(-45^\circ) \leftarrow \text{Use power triangles if unsure.} \\
 &= \boxed{-\frac{1}{2} \text{ VAR}}
 \end{aligned}$$

2. $i_b(t)$:

$$\begin{aligned}
 P_a &= V_{rms} \cdot I_{rms} \cos(\theta_v - \theta_i) \\
 &= \left(\frac{\sqrt{5}}{\sqrt{2}}\right) \left(\frac{\sqrt{2}}{\sqrt{2}}\right) \cos(26.57^\circ - 45^\circ) \\
 &= \boxed{\frac{3}{2} W} \\
 Q_a &= \boxed{-\frac{1}{2} \text{ VAR}}
 \end{aligned}$$

3. For R :

$$\begin{aligned}
 P_R &= V_{rms} \cdot I_{rms} = R I_{rms}^2 = 1 \cdot \left(\frac{\sqrt{2}}{\sqrt{2}}\right)^2 = \boxed{1 W} \\
 Q_R &= 0
 \end{aligned}$$

4. For L :

$$P_L = 0$$

$$Q_L = V_{rms} \cdot I_{rms} = \left(\frac{\sqrt{2}}{\sqrt{2}}\right) \left(\frac{\sqrt{2}}{\sqrt{2}}\right) = \boxed{1 \text{ VAR}}$$

Could have also used: $Q = \times I_{rms}^2 = \omega L I_{rms}^2$ Hilroy

S. For C:

$$P_C = 0$$

$$Q_C = V_{ms} \cdot I_{ms} \cdot \sin(\theta_v - \theta_i)$$

$$= \left(\frac{1}{\sqrt{2}}\right) \left(\frac{2}{\sqrt{2}}\right) \sin(-90^\circ)$$
$$= \boxed{-1 \text{ VAR}}$$

Recogniz.

$$Q = X I_{ms}^2 = -\frac{1}{\omega_C} I_{ms}^2$$

Note:

$$\underline{\sum P = 0} \quad , \quad \underline{\sum Q = 0}$$